


## UNIT # 10

## ELECTROMAGNETIC INDUCTION &amp; ALTERNATING CURRENT

## EXERCISE -I

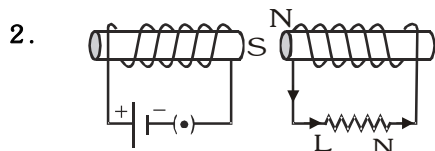1. Total change in flux = Total charge flown through the coil resistance

$$= \left( \frac{1}{2} \times 4 \times 0.1 \right) \text{ Resistance} = 0.2 \quad 10 = 2 \text{ Webers}$$



3.  $e = \left| -\frac{d\phi}{dt} \right| = Na^2 \frac{dB}{dt} = 5 \text{ volt}$


4.  $e = \left| -\frac{d\phi}{dt} \right| = NA \frac{dB}{dt} = (100)(40 \times 10^{-4}) \left( \frac{6-1}{2} \right)$   
 $= 0.8 \text{ volt} \approx 1 \text{ volt}$

5.  $q = \frac{\Delta\phi}{R} = \frac{NBA}{R} \Rightarrow B = \frac{qR}{NA}$


6.  $\phi = \pi r^2 B \Rightarrow e = \frac{d\phi}{dt} = (2\pi r B) \frac{dr}{dt}$

7.  $W = \int Q \vec{E} \cdot d\vec{\ell} = Q \int \vec{E} \cdot d\vec{\ell} = QV$

8.  $\frac{d\phi}{dt} = \oint \vec{E} \cdot d\vec{r} \Rightarrow -\alpha A = \oint \vec{E} \cdot d\vec{r}$

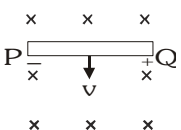9.   $e = B (2R) v = 2Brv$

10. According to Lenz's law

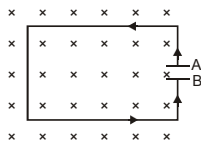

$\Rightarrow$  Plate B will become positively charged.

11.  $I = \frac{\frac{1}{2} B \omega \ell^2}{R}$

All spokes are in parallel

12.  $W = F\ell = N(I\ell B)\ell = N \left( \frac{NB\ell v}{R} \right) \ell^2 B = \frac{N^2 B^2 \ell^4}{tR}$

$$\therefore t = \frac{\ell}{v} \therefore W = \frac{N^2 B^2 A^2}{Rt} = 0.1 \text{ mJ}$$


13.  $I_1 = \frac{\varepsilon}{R_1} = \frac{\frac{1}{2} B \omega r^2}{R_1} = \frac{B \omega r^2}{2R_1}$

14.  $I\ell B > mg \Rightarrow I\ell B < mg$


15.  $\phi = NBA \cos \omega t$

$$\therefore e = -\frac{d\phi}{dt} = NBA\omega \sin \omega t \Rightarrow e_{\max} = NBA\omega$$

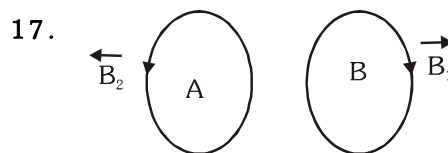
16.  $e = L \frac{\Delta I}{\Delta t} \Rightarrow L = \frac{e}{\Delta I / \Delta t} = \frac{8}{(4/0.05)} = \frac{8}{80} = 0.1 \text{ H}$



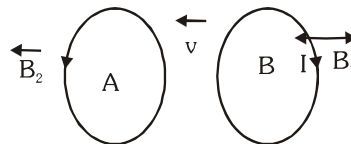$I$  increases  $B_1$  increases  
 So from Lenz's law  
 Current in A is clockwise



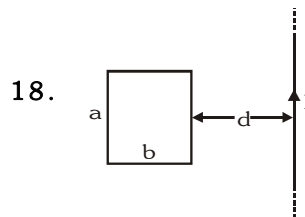$I$  same and flux linked with A increases  
 So from Lenz's law current in A clockwise




$$\therefore \phi = MI \text{ but } \phi = \int_d^{d+b} \frac{\mu_0 I}{2\pi x} (adx) = \frac{\mu_0 Ia}{2\pi} \ln \left( \frac{d+b}{d} \right)$$

$$\Rightarrow M = \frac{\mu_0 a}{2\pi} \ln \left( \frac{d+b}{d} \right) \Rightarrow M \propto a$$

19. Work done  $= LI_0^2 = (0.04) (5)^2 = 1.0 \text{ J}$

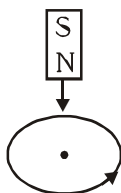20. According to Lenz's law current in loop as shown in figure due to this current, a magnetic force  $F_m$  is acted on bar magnetic if  $\phi$  is the acceleration of the bar magnet then



$$ma = mg - F \quad a = g - F/m \therefore a < g$$

21.  $100 = V_R + V_L$  But  $V_R = (4000)(15 \times 10^{-3}) = 60 \text{ volt}$   
 $\Rightarrow V_L = 40 \text{ volt}$


22.  $\frac{L}{R_1} = 2 \times 10^{-3}$  &  $\frac{L}{R_1 + R_2} = 0.5 \times 10^{-3}$   
 $\Rightarrow \frac{90 + R_1}{R_1} = 4 \Rightarrow R_1 = 30 \Omega, L = 60 \text{ mH}$

23. Here  $I_0 = \frac{E}{R} = \text{constant}$   
 $\Rightarrow$  We can't change E or R.

For curve 2 time constant  $\frac{L}{R}$  is more

24.  $I = I_0(1 - e^{-t/\tau}) \Rightarrow \frac{I_0}{2} = I_0(1 - e^{-t/\tau})$   
 $\Rightarrow t = \tau \ln 2 = \frac{L}{R} \ln 2 = \left( \frac{300 \times 10^{-3}}{2} \right) (0.693) = 0.1 \text{ s}$

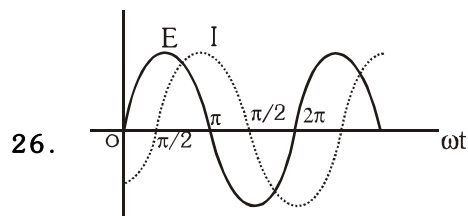25. Average value = 0  
 rms value =  $V_0$



E reaches at maximum value at  $\frac{\pi}{2}$  phase before  
 I reaches at its peak value at phase  $\pi$ .  
 So E is leads I by  $\frac{\pi}{2}$  So E is leads I by  $\frac{\pi}{2}$

27.  $I_{\text{rms}} = \sqrt{\frac{\int I^2 dt}{\int dt}} = \sqrt{\frac{\int_0^4 4t^2 dt}{\int_0^4 dt}} = \sqrt{\frac{(2t^3)_0^4}{(t)_0^4}} = \sqrt{12} = 2\sqrt{3} \text{ A}$

28. Ac ammeter reads rms value  
 dc ammeter reads average value

29.  $I_{\text{rms}} = \sqrt{\langle (I_0 + I_1 \sin \omega t)^2 \rangle} = \sqrt{\langle I_0^2 + I_1^2 \sin^2 \omega t + 2I_0 I_1 \sin \omega t \rangle}$   
 $= \sqrt{I_0^2 + \frac{I_1^2}{2}} = \sqrt{I_0^2 + 0.5 I_1^2}$

30. Impedance =  $\sqrt{R^2 + (\omega L)^2}$   
 At low frequency  $\omega \rightarrow 0$   
 so impedance  $\rightarrow R$   
 At high frequency  $\omega \rightarrow \infty$   
 so impedance  $\rightarrow \omega L$

31.  $R = \frac{V^2}{P} = \frac{(10)^2}{20} = 5 \Omega$   
 In AC circuit

$$P = VI \cos \phi = \frac{V^2}{Z} \cos \phi = \left( \frac{V^2}{Z} \right) \left( \frac{R}{Z} \right)$$

$$\Rightarrow 10 = \frac{(10)^2 (5)}{(5)^2 + (\omega L)^2} \Rightarrow \omega L = 5 \Omega$$

$$\Rightarrow \omega = \frac{5}{L} \Rightarrow f = \frac{\omega}{2\pi} = \frac{5}{2\pi L}$$

$$= \frac{5}{2 \times 3.14 \times 10 \times 10^{-3}} = 80 \text{ Hz}$$

32.  $X_c = \frac{1}{\omega c} = \frac{1}{2\pi f c}$

33.  $\phi = \tan^{-1} \left( \frac{X_c}{R} \right)$

34.  $Z = \sqrt{R^2 + X^2}$

If X is capacitive  $X = \frac{1}{\omega C}$

35.  $\phi = \tan^{-1} \left( \frac{X}{R} \right) = \tan^{-1} \left( \frac{\omega L}{R} \right)$   
 $= \tan^{-1} \left( \frac{200 \times 1}{200} \right) = \tan^{-1}(1) = 45$

36.  $\therefore \frac{\Delta \phi}{2\pi} = \frac{\Delta T}{T} \therefore \frac{\pi/4}{2\pi} = \frac{\Delta T}{T} \Rightarrow \Delta T = \frac{T}{8}$


but  $T = \frac{1}{50} \text{ s} \Rightarrow \Delta T = \frac{1}{400} \text{ s} = 2.5 \text{ ms}$

37.  $R = \frac{V}{I} = \frac{100}{25} = 4 \Omega$

$$\sqrt{R^2 + (\omega L)^2} = \frac{V}{I} = \frac{100}{20} = 5 \Rightarrow \omega L = 3 \Omega$$

38. Here  $V_L = V_C$   
 $\Rightarrow$  Resonance condition  
 $\Rightarrow$  Voltage across LC combination remains same

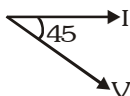39.  $\tan 45 = \frac{X_c - X_L}{R} \Rightarrow R = \frac{1}{2\pi f c} - 2\pi f L$



$$\Rightarrow R + 2\pi fL = \frac{1}{2\pi fC} \Rightarrow C = \frac{1}{2\pi f(2\pi fL + R)}$$

$$40. V_L - V_C = 50 - 50 = 0$$

$$41. \text{ Resonant frequency } \omega = \frac{1}{\sqrt{LC}}$$

$$42. V_L = IX_L = \left(\frac{V}{R}\right)(\omega L)$$

$$= \left(\frac{V}{R}\right)\left(\omega \times \frac{1}{\omega^2 C}\right) = \frac{V}{\omega RC} = \frac{100}{200 \times 10^3 \times 2 \times 10^{-5}}$$

$$= 250 \text{ volt}$$

$$43. V_4 = V_L + V_C = 0$$

$$44. V_R = 100 \text{ V}, I_R = \frac{V_R}{R} = \frac{100}{50} = 2 \text{ A}$$

45. Circuit will be capacitive if  $X_C > X_L$   
 Circuit will be inductive if  $X_L > X_C$

$$46. \text{ Reading of voltmeter} = 0 \text{ as } V_L = V_C$$

$$\text{Reading of ammeter} = \frac{V}{R} = \frac{240}{30} = 8 \text{ A}$$

$$47. \text{ Here } \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{5 \times 10^{-3} \times 50 \times 10^{-6}}} = 2000 \text{ rad/s}$$

$$\Rightarrow \omega = \frac{1}{\sqrt{LC}}$$

so resonance condition

$$\Rightarrow I = \frac{V}{R} = \frac{20/\sqrt{2}}{6+4} = \sqrt{2} = 1.4 \text{ A}$$

$$\text{and reading of voltmeter} = (I)(4) = 4\sqrt{2} = 5.6 \text{ V}$$


$$48. P = VI \cos \phi = \left(\frac{E_0}{\sqrt{2}}\right)\left(\frac{I_0}{\sqrt{2}}\right)\cos\left(\frac{\pi}{2}\right) = 0$$

$$49. \phi = \tan^{-1}\left(\frac{\omega L}{R}\right) = \tan^{-1}\left(\frac{2\pi \times 50 \times 0.7}{220}\right) = \tan^{-1}(1) = 45^\circ$$

wattless current =  $I_{\text{rms}} \sin \phi$

$$I = \frac{V}{Z} \frac{1}{\sqrt{2}} = \frac{220}{220\sqrt{2}} \frac{1}{\sqrt{2}} = \frac{1}{\sqrt{2}} \frac{1}{\sqrt{2}} \text{ A} = \frac{1}{2} \text{ A}$$
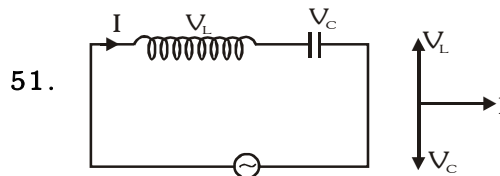
$$50. L \frac{di}{dt} = \frac{q}{C} \Rightarrow \left(\frac{di}{dt}\right)_{\text{max}} = \frac{q_0}{LC}$$




$$52. \text{ For LC circuit } q = q_0 \cos \omega t,$$

$$i = q_0 \omega \cos\left(\omega t + \frac{\pi}{2}\right)$$

According to given condition

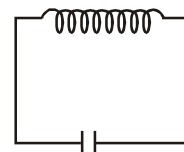
$$\frac{q^2}{2C} = \frac{1}{2} Li^2 \Rightarrow q = \frac{Q}{\sqrt{2}}$$



$$54. \phi = (\pi R^2)B = \pi B(R_0 + t)^2$$

$$\Rightarrow \frac{d\phi}{dt} = 2\pi B(R_0 + t) \text{ anticlockwise}$$
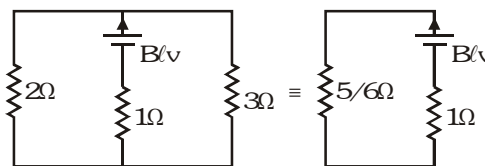
$$55. I = \frac{B \ell v}{1 + 6/5} = \frac{(0.1)(0.1)(1)}{11/5} = \frac{5}{1100} = \frac{1}{220} \text{ A}$$



$$56. e = -L \frac{di}{dt}, -\frac{di}{dt} \text{ is more for 1}$$

57. Dimension based : Check yourself.

$$58. I^2 R = P \Rightarrow R = \frac{P}{I^2} = \frac{\frac{1}{2} LP}{\frac{1}{2} LI^2} = \frac{LP}{2U} \Rightarrow \frac{L}{R} = \frac{2U}{P}$$

$$59. V_R = \sqrt{10^2 - 8^2} = 6 \text{ volt}$$

$$\phi = \tan^{-1}\left(\frac{\omega L}{R}\right) = \tan^{-1}\left(\frac{V_L}{V_R}\right) = \tan^{-1}\left(\frac{8}{6}\right) = \tan^{-1}\left(\frac{4}{3}\right)$$


60.  $i = 2 \sin 100\pi t + 2 \sin(100\pi t) \cos 30$   
 $+ 2 \cos(100\pi t) \sin 30$

$= (2 + \sqrt{3}) \sin 100\pi t + \cos(100\pi t)$


$I_{\text{rms}} = \sqrt{\langle i^2 \rangle} = \sqrt{\left( (2 + \sqrt{3})^2 \times \frac{1}{2} + 1 \times \frac{1}{2} \right)} = \sqrt{7.5 + 4\sqrt{3}}$

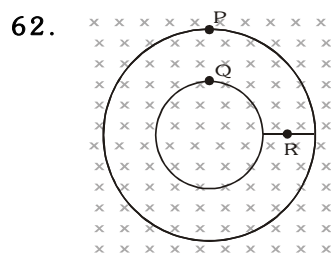61. Old power factor  $= \frac{R}{\sqrt{R^2 + (3R)^2}} = \frac{1}{\sqrt{10}}$

New power factor  $= \frac{R}{\sqrt{R^2 + (2R)^2}} = \frac{1}{\sqrt{5}}$



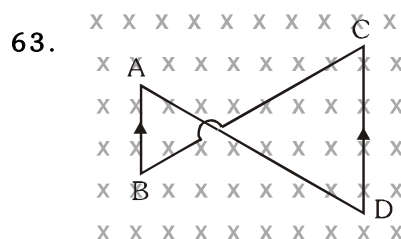$I_P$  &  $I_Q \rightarrow$  clockwise  $I_R = 0$



64.  $q_A = + (B\ell v) C = (4) (1) (20) (10 \cdot 10^{-6}) = 800 \mu\text{C}$   
 $q_B = -q_A = -800 \mu\text{C}$

65.  $\frac{E}{R_1} = \frac{E}{R_2} \Rightarrow R_1 = R_2, \frac{L_2}{R_2} > \frac{L_1}{R_1} \Rightarrow L_2 > L_1$

## EXERCISE -II

1.  $e = -\frac{d\phi}{dt}$  [where  $\phi = \vec{B} \cdot \vec{A}$ ]  $e = \frac{d}{dt} (BA \cos \theta)$   
 either  $\theta, A$  or  $B$  should be changed for induced e.m.f.


2. Total charge transferred  $= \frac{\Delta\phi}{R}$

It is independent of time

$\phi = \vec{B} \cdot \vec{A} \Rightarrow \int d\phi = \int_a^{2a} \frac{\mu_0 i}{2\pi x} dx$

$\Delta\phi = \phi - (-\phi) = 2\phi$

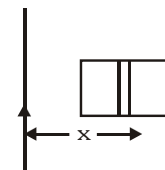$\Rightarrow \phi = \frac{\mu_0 ia}{2\pi} \ln 2 \Rightarrow q = \frac{\mu_0 ia \ln(2)}{\pi r}$



3.  $e = Bv\ell \Rightarrow \int_0^e de = \int_a^b \frac{\mu_0 i}{2\pi x} v dx$

$\Rightarrow e = \frac{\mu_0 iv}{2\pi} \ln(b/a) \Rightarrow i_1 = \frac{\mu_0 iv}{2\pi R} \ln(b/a)$

Force ( $\vec{F}$ )  $= Bi\ell = b \Rightarrow \int df = \int_a^b \frac{\mu_0 i}{2\pi x} i_1 dx$

$f = \frac{\mu_0 i}{2\pi} \ln\left(\frac{b}{a}\right) i_1 = \left[ \frac{\mu_0 IV}{2\pi} \ln\left(\frac{b}{a}\right) \right]^2 \frac{V}{R}$

4.  $\phi = BA = \frac{\mu_0 ir^2}{2(R^2 + x^2)^{3/2}} \pi R^2$

$e = \frac{d\phi}{dt} = -\frac{3\mu_0 ir^2 R^2 \pi x}{(R^2 + x^2)^{5/2}}$

For  $e$  to be maximum

$\frac{d(e)}{dx} = 0 \Rightarrow x = \frac{R}{2}$

5.  $\phi \propto I \Rightarrow LI = \phi \Rightarrow i = \frac{\Delta\phi}{L} \Rightarrow i = \frac{2B\pi R^2}{L}$

6.  $e = \frac{B\omega L^2}{2}$

effective length of the wire frame is  $2R$

$\Rightarrow e = 2B\omega R^2$

7.  $\omega = \frac{1}{2\pi} \frac{1}{\sqrt{LC}} \Rightarrow \omega = \frac{1}{6\pi\sqrt{LC}}$

8.  $\tan 60 = \frac{X_C}{R}$  Also  $\tan 60 = \frac{X_L}{R}$  is  $X_C = X_L = \sqrt{3} R$   
 series L-C-R is in resonating condition

$I = \frac{V}{R} = 2A$

$P = I^2 R = 4 \cdot 100 = 400W$

9.  $P = \frac{V^2}{R} \Rightarrow R = \frac{V^2}{P} = 100\Omega$

with AC source

$$P = \left(\frac{V}{Z}\right)^2 R \Rightarrow Z = 200\Omega$$

$$Z^2 = R^2 + \omega^2 L^2 \Rightarrow L = \frac{\sqrt{Z^2 - R^2}}{\omega} = \frac{\sqrt{3}}{\pi} \text{ H}$$

10.  $\frac{i_1}{i_2} = \frac{1}{4} \Rightarrow \frac{W_1}{W_2} = \frac{1}{4}; \Rightarrow \frac{V_1}{V_2} = 4$

11. Minimum value of impedance is for

$$X_L = X_C \Rightarrow \frac{1}{\omega C} = \omega L \Rightarrow L = \frac{1}{\omega^2 C} = 0.36 \text{ mH}$$

12. In DC (act as open circuit)

$$\text{So } R = \frac{250}{1} = 250 \Omega$$

$$\text{At resonance } \omega L = \frac{1}{\omega C}$$

$$\frac{1}{4500C} = 4500L \dots(i)$$

$$V = V_C - V_L = V_R$$

$$I_2 \left( \frac{1}{\omega C} - \omega L \right) = V \Rightarrow I_1 R = V$$

$$\text{Here } I = \sqrt{I_1^2 + I_2^2} \Rightarrow I^2 = \frac{V^2}{R^2} + \frac{V^2}{\left( \frac{1}{\omega C} - \omega L \right)^2}$$

$$\Rightarrow \frac{(5/4)^2}{(250)^2} = \frac{1}{(250)^2} + \frac{1}{(1/\omega C - \omega L)^2}$$

$$\frac{1}{\omega C} - \omega L = \frac{4}{3} \times 250 \text{ here } \omega = 2250 \text{ rad/sec}$$


$$\text{So, } \frac{1}{2250C} = \frac{4}{3} \times 250 + 2250L \dots(ii)$$

From (i) & (ii) :

$$2 = \frac{\frac{4}{3} \times 250 + 2250L}{4500L}$$

$$9000L = \frac{4}{3} \times 250 + 2250L$$
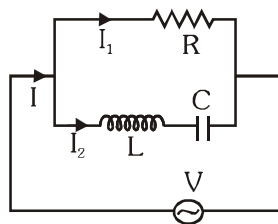
$$L = \frac{4}{3} \times \frac{250}{6750} = 0.0494 \text{ H}$$



$$C = \frac{1}{(4500)^2 \times 0.0494} = 10^{-6} \text{ F}$$

13.  $\phi = \left[ \frac{\mu_0 (e/T)}{2R} \right] \pi r^2 \Rightarrow \frac{d\phi}{dt} = \frac{\mu_0 e \pi r^2}{2RT^2}$

$$\Rightarrow e = \frac{\mu_0 e \pi r^2 \alpha}{2R(2\pi)} = \frac{\mu_0 e \alpha r^2}{4R}$$

14.  $e = \frac{AdB}{dt}$

$$10 = (10 \times 10^{-2})^2 \frac{(4-0)}{\Delta t} \Rightarrow \Delta t = 20 \text{ ms}$$

15.  $\phi = \vec{B} \cdot \vec{A} \Rightarrow \phi = \int \frac{\mu_0 i_0 e^{-t/\tau}}{2\pi x} b \, dx$

$$\Rightarrow \phi = \frac{\mu_0 i_0 e^{-t/\tau}}{2\pi} b \ln\left(\frac{a+d}{d}\right)$$

$$\Rightarrow e = \frac{d\phi}{dt} = \frac{\mu_0 i_0 e^{-t/\tau} b}{\tau 2\pi} \ln\left(\frac{a+d}{d}\right)$$

16.  $\phi = at(T-t) \Rightarrow \frac{d\phi}{dt} = aT - 2at$

$$\Rightarrow i = \frac{d\phi}{Rdt} = (aT - 2at)$$

$$\text{Heat} = \int_0^T (aT - 2at)^2 R dt$$

$$= \left[ a^2 T^2 t + 4a^2 \frac{t^3}{3} - 4a^2 T \frac{t^2}{2} \right]_0^T R$$


$$= \left[ a^2 T^3 + \frac{4a^2 T^3}{3} - 2a^2 T^3 \right] R \quad \text{Heat} = \frac{a^2 T^3}{3R}$$

17. Area in the magnetic field is given by

$$A = x^2; \phi = Bx^2$$

$$\frac{d\phi}{dt} = 2Bx \left( \frac{dx}{dt} \right) = 2Bvx$$
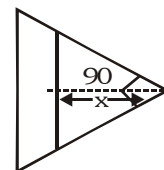
$$i = \frac{1}{R} \frac{d\phi}{dt} = \frac{2Bv^2 t}{R}, \quad i \propto t$$




18. No induced current in the loop therefore No force acts over the loop. Work done on the loop will be zero

19. Equivalent circuit diagram is as shown

$$\Rightarrow i = \frac{4e}{4r} = \frac{e}{r} = \frac{Bv\ell}{r\ell}$$

$$\Rightarrow i = \frac{Bv}{r}$$

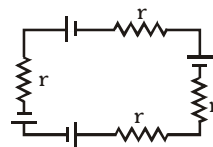

20.  $e = B\ell v$   
where all the three should be perpendicular to each other

$$e = \vec{B}(\vec{\ell} \times \vec{v}) \Rightarrow e = (3\hat{j} + 4\hat{k}) [(3\hat{i} + 4\hat{j}) \times 2\hat{i}]$$

$$= (3\hat{j} + 4\hat{k})(8\hat{k}) \Rightarrow e = 32 \text{ volt}$$


21. As capacitor blocks the current there will be no current in the circuit HKDE

22.  $e = \frac{B\omega\ell^2}{2}$

effective length for the given diagram is


$$l_{\text{eff}}^2 = \ell^2 + L^2 \Rightarrow e = \frac{B\omega(\ell^2 + L^2)}{2}$$

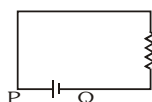23. By Fleming's left hand rule equivalent circuit diagram is as shown current will be P to Q In the disc




24.  $e = L \frac{di}{dt} \Rightarrow 2 = \frac{4(5-0)}{\Delta t} \Rightarrow \Delta t = 10 \text{ sec}$

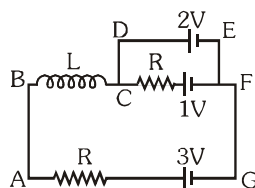25. In loop CDEF current is independent of the time as current will remain  $\frac{V}{R}$  all the time



$\therefore$  Circuit equivalent can be considered as

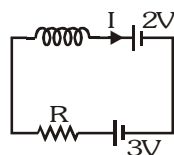current at any time  $= \frac{V_0}{R} [1 - e^{-\frac{Rt}{L}}]$



By superimposing the two currents the net current in it will be

$$i = \frac{V_0}{R} - \frac{V_0}{R} e^{-\frac{Rt}{L}} - \frac{V_0}{R} = -\frac{V_0}{R} e^{-\frac{Rt}{L}}$$

26. Decay of current in L-R circuit is given by

$$-\frac{L di}{dt} - iR = 0$$

$$i = -\frac{L}{R} \frac{di}{dt} \Rightarrow i = i_0 (1 - e^{-\frac{Rt}{L}})$$

$$\text{Heat (ऊष्मा)} = \int L^2 R_2 dt = \frac{E^2}{R_1} R$$

OR

Heat produced = energy stored in inductor

$$= \frac{1}{2} L \left( \frac{E}{R_1} \right)^2 = \frac{LE^2}{2R_1^2}$$

27.  $u = \frac{1}{2} LI^2 \Rightarrow u = 32 \text{ Joule}$

$$L = ?, I = 4A$$

$$L = 4H, P = i^2 R \Rightarrow R = 20 \text{ ohm}$$


Time (समय)  $= \frac{L}{R} = 0.2 \text{ sec}$

29. As current in the circuit is given by  $\frac{V_0}{R}$

$$\Rightarrow X_L = X_C = \omega L = 100\pi \quad \frac{1}{\pi} = 100\Omega$$

$$\cos \theta = \frac{R}{Z} = \frac{1}{\sqrt{2}}$$

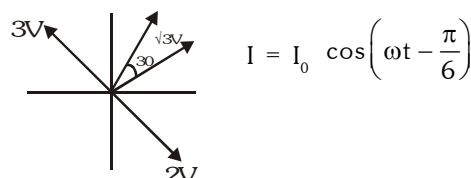30.  $V = 2V_0 \cos\left(\omega t + \frac{\pi}{6}\right)$  as voltage across inductor is more circuit behaves like an inductive circuit is current lags voltage by an amount  $30^\circ$ .



31. For (L - R) circuit

$$\cos \theta = \frac{3}{5} \Rightarrow \theta = 53^\circ \Rightarrow X_L = \frac{4}{3} R$$

For (C - R) circuit


$$\cos \theta = \frac{1}{2} \Rightarrow \theta = 60^\circ \Rightarrow X_C = \sqrt{3} R_2$$

In L-C-R power factor is  $i$  i.e. reactance is zero

$$X_L = X_C \Rightarrow \frac{4}{3} R_1 = \sqrt{3} R_2 \Rightarrow \frac{R_2}{R_1} = \frac{4}{3\sqrt{3}}$$

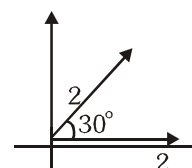32.  $I_0 = \sqrt{I_1^2 + I_2^2 + 2I_1 I_2 \cos 30^\circ}$

$$= \sqrt{4 + 4 + 8 \times \frac{\sqrt{3}}{2}}$$




$$\Rightarrow I_0 = 2\sqrt{2 + \sqrt{3}} \quad I_{\text{eff}} = \frac{I_0}{\sqrt{2}} \Rightarrow \sqrt{\frac{2 + \sqrt{3}}{2}}$$

33.  $I_{\text{rms}} = \int_0^2 \sin \omega t R dt \Rightarrow I_1 = I_2$

and current in the  $I_3$  more than  $I_1 = I_2$   
 $I_3 > I_1 = I_2 > I_4$

34. If  $I_2=0$  and P moves towards Q, then according to Lenz law a current in opposite as  $I_1$  is induced in Q. Same as  $I_1=0$  and Q moves towards P when  $I_1 \neq 0$ ,  $I_2 \neq 0$  are in opposite direction then the coils repels each others.

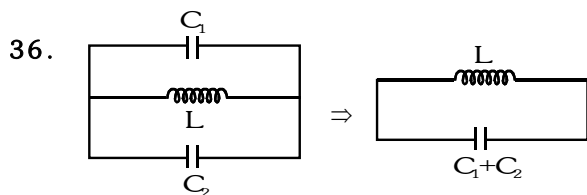35. No emf will be induced in any direction of its motion  
 $(\vec{\ell} \parallel \vec{B})$



We know  $q = q_m \cos \omega t$

$$i = q_m \omega \cos \left[ \omega t + \frac{\pi}{2} \right], i = i_0 \cos \left( \omega t + \frac{\pi}{2} \right)$$

$$\text{Maximum current } i_0 = q_m \omega \left[ \omega = \frac{1}{\sqrt{L(C_1 + C_2)}} \right]$$

Maximum charge on  $(C_1 + C_2)$

$$q_m = \frac{i_0}{\omega} = i_0 \sqrt{L(C_1 + C_2)}$$

Maximum charge on  $C_1$

$$= \frac{C_1}{C_1 + C_2} \times i_0 \sqrt{L(C_1 + C_2)} = i_0 C_1 \sqrt{\frac{L}{C_1 + C_2}}$$

37. Sudden increase in the e.m.f. cause the spark in the inductor

38. In absence of L whole emf of B goes on lamp and lamp will glow with full brightness instantaneously but in presence of L some emf is induced in L. Voltage drop on P decrease and brightness ↓.

39.  $\phi_1 = M I_2, 4 = 2 I_2 \Rightarrow I_2 = 2A$

40.  $I = \frac{V}{Z}$

$$X_L = 2\pi 50 \quad 2 = 200\pi$$

$$X_L = 2\pi(400) \quad 2 = 1600\pi$$

Z increases 8 times current decreases by 1/8


41.  $I_a$  is the induced current of  $i_1$ , so the nature of  $i_1$  become should becomes opposite of  $i_a$  ie negative.

42. Charge on the capacitor  $Q = CV = C (Bv_0 \ell)$

As all the quantities are constant

$$\text{so } dQ = 0 \quad \text{Hence } i = \frac{dQ}{dt} = 0$$

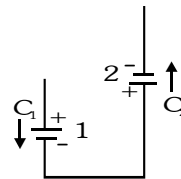43. Replace the induced emf's in the rings by cell



$$e_1 = B(2r) (2V) = 4BrV$$


$$e_2 = B(4r) (V) = 4BrV$$

$$V_2 - V_1 = e_2 + e_1 = 8BrV$$


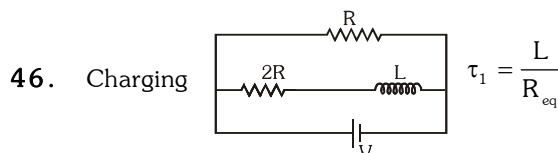
44.  $e = - \frac{d\phi}{dt} = - \frac{d}{dt} [BA \cos \theta] = - \frac{d}{dt} \left( B_0 \left( 1 + \frac{x}{a} \right) \right) d^2$

[ $\therefore$  Area of square =  $d^2$ ,  $\theta = \infty$ ]

$$= \frac{B_0 d^2}{a} \frac{dx}{dt} = \frac{B_0 d^2}{a} V_0 \quad (\vec{V} = V_0 \hat{i})$$



For determining R

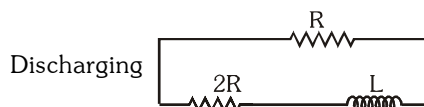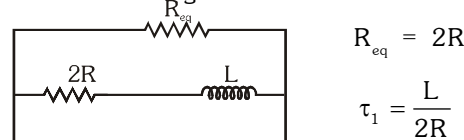

$$\tau_2 = \frac{1}{3R} \Rightarrow \frac{\tau_1}{\tau_2} = \frac{3}{2}$$

47. Energy per unit volume


$$= \frac{B^2}{2\mu_0} = \int \frac{1}{2\mu_0} \left( \frac{\mu_0 i r}{2\pi a^2} \right)^2 2\pi r dr$$

$$= \frac{1}{2\mu_0} \frac{\mu_0^2 i^2 r^2}{4\pi^2 a^4} \times 2\pi r dr = \frac{\mu_0 i^2}{4\pi a^4} \int_0^a r^3 dr$$

$$= \frac{\mu_0}{4\pi a^4} \times \frac{a^4}{4} = \frac{\mu_0 i^2}{16\pi}$$

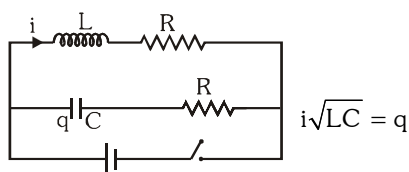48. Current through C and L would be equal after

$$\text{a time } t \text{ when } \frac{1}{2} Li^2 = \frac{q^2}{2C}$$



$$q = q_0 (1 - e^{-t/RC}), \quad i = \frac{q_0}{RC} e^{-t/RC}$$

$$\frac{q_0}{RC} e^{-t/RC} \sqrt{LC} = q_0 (1 - e^{-t/RC})$$

$$\frac{\sqrt{L/C}}{R} e^{-t/RC} = 1 - e^{-t/RC}$$

$$2e^{-t/RC} = 1 \Rightarrow e^{t/RC} = 2$$

$$\Rightarrow \frac{t}{RC} = \ln 2 \Rightarrow t = RC \ln 2$$

49.  $I_0 = 1.57$

Instantaneous voltage across capacitor

$$E = V_0 \sin \omega t, \quad V_0 = X I_0 = \frac{1}{2\pi f C} \times I_0$$

$$= \frac{1}{2\pi \times 50 \times 100 \times 10^{-6}} \times 1.57 \Rightarrow V_0 = 50$$

$$\therefore E = 50 \sin 100\pi t$$


50.  $I = \sqrt{I_1^2 + I_2^2}$

$$I^2 = \frac{(200)^2}{(100)^2} + \frac{V^2}{(X_L - X_C)^2}$$

$$= 4 + \frac{(200)^2}{(100)^2} = 4 + 4 = 8$$

$$\Rightarrow I = 2\sqrt{2} \Rightarrow I_{rms} = \frac{I}{\sqrt{2}} = 2$$

51.

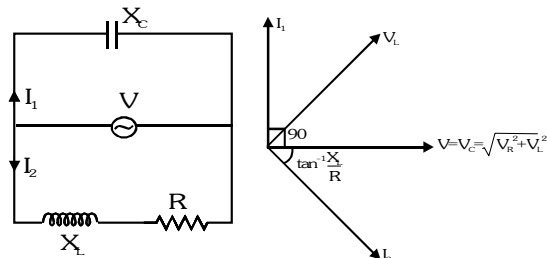

So phase difference between  $I_1$  and  $I_2$

$$= \frac{\pi}{2} + \tan^{-1} \frac{X_L}{R}$$

52. Time constant of L-R circuit is  $= \frac{L}{R}$

$$\text{From option (A)} = 2 \times \frac{\frac{1}{2} Li^2}{i^2 R} = \frac{L}{R}$$

53. The electric field force due to variable magnetic

$$\text{field} = \frac{1}{2} \times \vec{R} \times \frac{d\vec{B}}{dt} \times q = \frac{1}{2} eR \frac{dB}{dt}$$

$$\therefore \text{Acceleration} = \frac{1}{2m} eR \frac{dB}{dt}$$

54. Induced current

$$I = \frac{e}{R} = \frac{1}{R} \left( -\frac{nd\phi}{dt} \right) = \frac{-n(\omega_2 - \omega_1)}{5R} t$$

56.  $L = \frac{\mu_0 N^2 A}{L}; \quad N \quad 2\pi r = L$

As wire is fixed

$$\therefore N' 2\pi \frac{r}{2} - L = N 2\pi r \Rightarrow N' = 2N$$

$$\therefore i = \mu_0 \frac{(2N)^2 \times \pi \left( \frac{r}{2} \right)^2}{\frac{L}{2}} \Rightarrow L' = 2L$$

58.  $V_{rms} = \sqrt{\frac{\int_0^{T/4} V^2 dt}{\int_0^{T/4} dt}} = \sqrt{\frac{\int_0^{T/4} \left( \frac{4V_0}{T} t \right)^2 dt}{\int_0^{T/4} dt}}$

$$= \sqrt{\frac{4 \times 4V_0^2}{T^2} \times \frac{T^3}{16 \times 4 \times 3}} = \frac{V_0}{\sqrt{3}}$$

59. Average value  $= \frac{\text{Area}}{\text{time}} = 0$

(in 0-T interval)

60.  $I = \frac{V}{\sqrt{R^2 + \left( \frac{1}{\omega C} \right)^2}} \quad \& \quad \frac{I}{2} = \frac{V}{\sqrt{R^2 + \frac{1}{\left( \frac{\omega C}{3} \right)^2}}}$

$$\therefore (2)^2 = \frac{R^2 + \frac{9}{\omega^2 C^2}}{R^2 + \frac{1}{\omega^2 C^2}} \Rightarrow 4R^2 + \frac{4}{\omega^2 C^2} = R^2 + \frac{9}{\omega^2 C^2}$$

$$\Rightarrow 3R^2 = \frac{5}{\omega^2 C^2} \Rightarrow 3R^2 = 5X_C^2 \Rightarrow \sqrt{\frac{3}{5}} = \frac{X_C}{R}$$



## EXERCISE -III

## Match the column-I

$$V = 100 \sin(100t) \Rightarrow i = 10 \sin \left( 100t - \frac{\pi}{4} \right)$$

(A) Phase difference  $\left( \frac{\pi}{4} \right)$

$$\cos \theta = \frac{R}{Z} \Rightarrow Z = \sqrt{2}R ; \tan \theta = \frac{X_L}{R} \Rightarrow X_L = R$$

(B)  $I_0 = \frac{V_0}{Z} \Rightarrow Z = 10 \Omega \quad Z = \sqrt{R^2 + X_L^2}$   
 $\sqrt{R^2 + R^2} = 10 \Rightarrow R = 5\sqrt{2} \Omega = X_L$

$$X_L = \omega L = 5\sqrt{2} \Rightarrow L = \frac{1}{10\sqrt{2}}$$

(C) Average power =  $VL \cos \theta$

$$= \frac{100 \times 10}{2} \times \frac{1}{\sqrt{2}} = 250\sqrt{2}$$

## Match the column II

Peak value current in the circuit is given by

$$i_0 = \frac{V}{R_0}$$

$\Rightarrow$  If  $R$  will be less current will be maximum

Slope of  $i$  (v/s)  $t$  graph gives time constant is  $\frac{L}{R}$

(A) Graph III and IV denotes for ' $R_0$ ' and slope is more for III therefore  $R_0, L_0$  represent III and (IV) represent  $R_0, 2L_0$

(B) Similarly I and II denotes for ' $2R_0$ ' and slopes is more for 'I'

## Match the column III

(A)  $I_{rms} = \frac{I_0}{\sqrt{2}}$

$$I_{mean} \text{ for full cycle} = 0$$


$$I_{mean} \text{ for half cycle} = 0$$

$$I_{mean} \text{ for half cycle} = \frac{2I_0}{\pi}$$

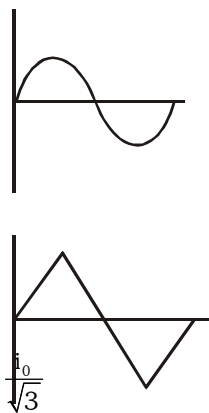(B)  $i = \frac{4i_0}{T} t$

$$i_r = \frac{16I_0^2}{T^2} \int_0^{T/2} t^2 R dt \Rightarrow i_{rms} = \frac{I_0}{\sqrt{3}}$$

$$i_{mean} = \frac{\text{Total Area}}{\text{Total time}} \Rightarrow i_{mean} = 0 \text{ for full cycle}$$




$$\Rightarrow i_{mean} = \frac{i_0 T_0 2}{4T_0} = \frac{i_0}{2} \text{ [for half cycle]}$$

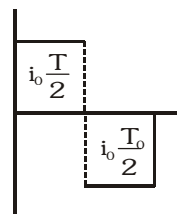(C)  $i_{mean} = \frac{\text{Total Area}}{\text{Total time}} = \frac{0}{T}$

$$\Rightarrow i_{mean} = 0$$


$$\Rightarrow i_{mean} = \frac{i_0 T_0 / 2}{T_0 / 2} = i_0$$



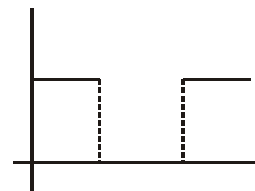(D)  $i_{mean} = \frac{\text{Total Area}}{\text{Total time}}$


$$i_{mean} = \frac{i_0 T_0 / 2}{T_0}$$

$$i_{mean} = \frac{i_0}{2} \Rightarrow i_{half \text{ cycle}} = \frac{i_0 T / 2}{T / 2} = i_0$$



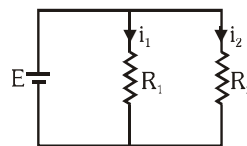
## Match the column (IV)

at  $t = 0$  at  $t = \infty$   $i_1 \frac{E}{R_1} (1 - e^{-\frac{R_1}{L}t})$



$$i_1 = 0$$
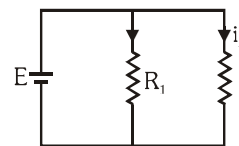
$$i_2 = \frac{E}{R_2} = \frac{18}{6} = 3A$$



$$i_2 = \frac{E}{R_2} = \frac{18}{3} = 6A$$

$$i_1 = \frac{18}{6} = 3A$$

## Match the column V

(A)  $\tan \theta = \frac{X_C}{R} \Rightarrow \frac{1}{\omega CR} = \frac{1}{10 \times 10^4 \times 10^{-6} \times 10}$

$$\tan \theta = 1 \Rightarrow \theta = \frac{\pi}{4}$$

(B)  $\tan \theta = \frac{X_L}{R}$  as  $R = 0 \Rightarrow \theta = \frac{\pi}{2}$

(C)  $\tan \theta = \frac{X_C}{R}$  as  $R = 0 \Rightarrow \theta = \frac{\pi}{2}$

(D)  $\tan \theta = \frac{X_C - X_L}{R}$  as  $R = 0 \Rightarrow \theta = \frac{\pi}{2}$

(E)  $\tan \theta = \frac{X_L}{R} = \frac{200 \times 5}{1000} \Rightarrow \theta = \frac{\pi}{4}$

## Match the column VI

(A)  $\frac{d\phi}{dt} = 5 \Rightarrow i = \frac{5}{10} \Rightarrow \frac{1}{2}$  Anticlockwise

(B)  $\frac{d\phi}{dt} = 0 \Rightarrow i = 0 = \text{zero}$

(C)  $\frac{d\phi}{dt} = -5 \Rightarrow i = -\frac{5}{10} = -\frac{1}{2} = \text{Clockwise}$

(D)  $\frac{d\phi}{dt} = 5 \Rightarrow \text{Anticlockwise}$

### Comprehension-1

1.  $f = Bi\ell \Rightarrow f = \frac{B^2 \ell^2 v}{R}$

$\Rightarrow 3.2 \times 10^{-5} = \frac{4 \times 10^{-4} \times 64 \times 10^{-4} \times v}{2}$

$\Rightarrow \frac{1}{40} \times 10^3 = v \Rightarrow 25 \text{ m/s}$

2.  $e = B\ell v = 2 \times 10^{-2} \times 8 \times 10^{-2} \times 25 = 4 \times 10^{-2} \text{ V}$

3.  $V = E - ir \Rightarrow V = B\ell v - \frac{B\ell v}{R}(R) \Rightarrow V = 3.6 \times 10^{-2} \text{ V}$

### Comprehension-2

1. By applying K.V.L.

For ABCDE

$\Rightarrow 18 - 6i \frac{di_1}{dt} = 0 \dots(i)$

By applying K.V.L.

for ABCFG

$\Rightarrow 18 - 6i - 3(i - i_1) = 0 \Rightarrow 18 - 9i + 3i_1 = 0$

$\Rightarrow i = \frac{18 + 3i_1}{9} \dots(ii)$


Substituting its value in equation (i)

$\Rightarrow 18 - 6 \left[ \frac{18 + 3i_1}{9} \right] - \frac{di_1}{dt} = 0 \Rightarrow 18 - 12 - 2i_1 = \frac{di_1}{dt}$


$\Rightarrow 2 \int_0^t dt = \int_2^{i_1} \frac{di_1}{3 - i_1} \Rightarrow -2t = \ln \left( \frac{3 - i_1}{3} \right) - \ln(1)$

$\Rightarrow 3 - i_1 = e^{-2t} \Rightarrow i_1 = 3 - e^{-2t}$

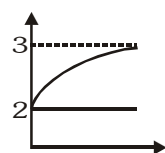2.  $V_1 + V_2 = V \Rightarrow 18 - 6e^{-2t} + V_2 = 18 \Rightarrow V_2 = 6e^{-2t}$



4.

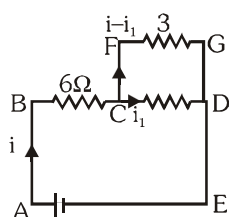

### Comprehension-3

1. M is same as that of L

$\frac{k}{m}$  is same as that of  $\frac{L}{LC}$

k is same as that of  $\frac{1}{C} \Rightarrow mk \rightarrow \frac{L}{C}$

### Comprehension-4

1.  $q = q_0 \sin(\phi) \dots(1)$

$\frac{dq}{dt} = q_0 \omega \cos(\phi) \Rightarrow \sqrt{5} = q_0 \omega \cos(\omega t + \phi)$

By dividing (1) and (2) we get

$\frac{4}{\sqrt{5}} = \frac{1}{\omega} \tan(\omega t + \phi) \tan(\phi) = \frac{2}{\sqrt{5}}$

from above equation  $\sin(\omega t + \phi) = \frac{2}{3}$

$Q = Q_0 \sin(\omega t + \phi) \Rightarrow 4 = Q_0 \left( \frac{2}{3} \right) \Rightarrow Q_0 = 6C$

2.  $(\omega t + \phi) = \frac{\pi}{2} \Rightarrow \omega t = \frac{\pi}{2} - \phi \Rightarrow t = 2 \left[ \frac{\pi}{2} - \sin^{-1} \left( \frac{2}{3} \right) \right]$

### Comprehension-5

1.  $\phi_1 = B(L^2 + \ell^2)$  as current in both direction are additive in nature while  $\phi_2 = B(L^2 - \ell^2)$  as current in both the loops are in opposite direction.


2. By lenz law in both the loop are in clock wise direction therefore it flows from b to a and d to c in both the loop.

3. Again by lenz law current in both direction should be clockwise but it is not possible therefore it is clockwise in bigger loop and in anticlockwise in smaller loop as e.m.f. due to bigger one is greater than smaller one

4.  $I_1 > I_2$

## EXERCISE -IV (A)


1.

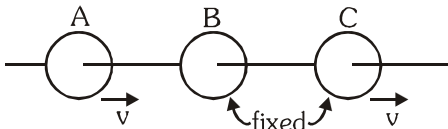

Due to current in C no change in  $\phi$  of B. So no induced current in B. But due to I in A,  $\phi$  is changing in B because A is moving towards B.  $\phi$  is changing (increasing) in B.


So according to Lenz's law direction of induced current in B will be such that it will try to decrease the  $\phi$  in B so current will be opposite in direction in B than A.

2.

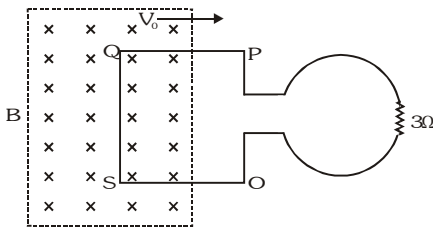

$$e = Bv\ell = IR \Rightarrow v = \frac{IR}{B\ell} = \frac{(1 \times 10^{-3})(4)}{(2)(10 \times 10^{-2})} = 0.02 \text{ ms}^{-1}$$

3.

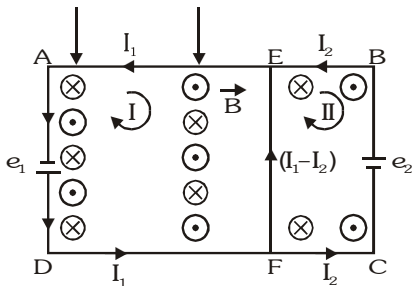

Refer to figure Electromotive force (emf) is induced in circuits I and II due to change of magnetic flux threading the circuits because magnetic field B is changing with time. As the areas enclosed by the circuits remain unchanged, the magnitude of the induced emf is given by

$$e = \frac{d\phi}{dt} = \frac{d}{dt}(BA) = \frac{AdB}{dt}$$

Area enclosed by circuit I is

$$A_1 = AD \quad AE = 1\text{m} \quad 1\text{m} = 1\text{m}^2.$$

Therefore, the emf induced in circuit I is

$$e_1 = 1\text{m}^2 \cdot 1 \text{ Ts}^{-1} = 1 \text{ Tm}^2\text{s}^{-1} = 1\text{V}$$

Area enclosed by circuit II is

$$A_2 = EB \quad EF = 0.5 \text{ m} \quad 1\text{m} = 0.5 \text{ m}^2$$

$\therefore$  Induced emf in circuit II is

$$e_2 = 0.5 \text{ m}^2 \cdot 1 \text{ Ts}^{-1} = 0.5 \text{ V}$$

Let  $I_1$  and  $I_2$  be the induced currents in circuits I and II respectively. From Lenz's law, the directions of these currents must be such that they oppose the increase in currents. In other words, the directions of the current in circuits I and II must be such that

they produced a magnetic field which is normal to the plane of the paper but point upwards, i.e. towards the reader. This requires that current  $I_1$  and  $I_2$  flow in the directions shown in the figure.

Since the resistance per unit length is  $1 \Omega\text{m}^{-1}$ , the resistance of wires AD, AE, DF and EF are  $1 \Omega$  each and those of wires EB, BC and FC are  $0.5 \Omega$  each. Applying Kirchhoff's loop rule to loop I (AEFDA),

$$I_1 - 1 + (I_1 - I_2) \times 1 + I_1 \times 1 + I_1 \times 1 - e_1 = 0$$

$$\text{or } 4I_1 - I_2 = e_1 = 1 \text{ volt} \dots\dots\dots(1)$$

Applying Kirchhoff's loop rule to loop I (BCFCB), we have

$$e_2 - I_2 \cdot 1 - I_2 \cdot 0.5 - (I_1 - I_2) \cdot 1 - I_2 \cdot 0.5 = 0$$

$$\text{or } 3I_2 - I_1 = e_2 - 0.5 \text{ volt} \dots\dots\dots(2)$$

Solving equation (1) and (2), we get

$$I_1 = \frac{7}{22} \text{ and } I_2 = \frac{3}{11} \text{ A.}$$

Referring to figure, the current in segment AE =  $I_1$

$$= \frac{7}{22} \text{ A in the direction from E to A, the current}$$

$$\text{in segment BE} = I_2 = \frac{3}{11} \text{ A in the direction from B}$$

$$\text{to E and the current in segment EF} = I_1 - I_2 = \frac{7}{22}$$

$$= \frac{3}{11} = \frac{1}{22} \text{ A in the direction from F to E.}$$

4.

$$\therefore q = \frac{\Delta\phi}{R} = \frac{NBA}{R} \therefore B = \frac{qR}{NA}$$

$$= \left( \frac{\pi}{100} \right) \left( \frac{895 + 5}{100 \times \pi(3 \times 10^{-2})^2} \right) = 10^2 \text{ T}$$

5.

$$\text{Induced emf in coil } e = M \frac{dI}{dt}$$

$$\text{Mutual inductance of system } M = \frac{\mu_0 N_1 N_2 A}{\ell}$$

$$\text{where } (\overline{\text{अहाँ}}) n = \frac{N_1}{\ell}, N_2 = N, A = \pi R^2$$

$$\Rightarrow M = \mu_0 n N (\pi R^2)$$

$$\text{Therefore } e = \mu_0 n N (\pi R^2) \frac{d}{dt} (I_0 \sin \omega t)$$

$$\Rightarrow \mu_0 n N (\pi R^2) I_0 \omega \cos \omega t$$

6.

- (i) Clockwise  $B \uparrow, \phi \downarrow$
- (ii) Anticlockwise  $B \downarrow, \phi \downarrow$
- (iii) Anticlockwise  $A \downarrow, \phi \downarrow$
- (iv) Clockwise  $A \uparrow, \phi \uparrow$

7.

$$\text{Induced emf in the loop} = B_1 v \ell - B_2 v \ell = (B_1 - B_2)$$

$$v \ell \left[ \frac{\mu_0 I}{2\pi x} - \frac{\mu_0 I}{2\pi(x+a)} \right] \text{ (v) (a)} = \frac{\mu_0 I}{2\pi} \left( \frac{a^2 v}{x(x+a)} \right)$$

$$= \frac{2 \times 10^{-7} \times 50 \times (0.1)^2 \times 10}{0.2 \times 0.3} = \frac{50}{3} \mu\text{V}$$

8. (i) Maximum Current

$$I_{\text{max}} = \frac{e_{\text{max}}}{R} = \frac{NBA\omega}{R} = \frac{50 \times 0.3 \times 2.5 \times 60}{500} = 4.5 \text{ A}$$

- (ii) Flux is maximum when plane of coil is at 90° to the magnetic field. Flux is zero when plane of coil is at 0° to the magnetic field.  
(iii) Yes it will work because  $\phi$  related to coil continuous in change.


- 9 Induced emf in primary coil

$$E_p = \frac{d\phi}{dt} = \frac{d}{dt} (\phi_0 + 4t) = 4 \text{ volt}$$

Induced emf in secondary coil

$$\frac{E_s}{E_p} = \frac{N_s}{N_p}$$
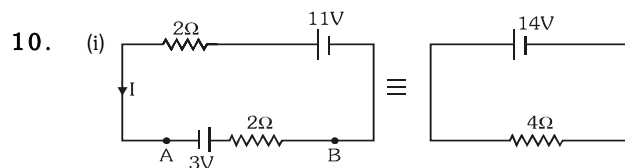
$$\Rightarrow E_s = \left( \frac{N_s}{N_p} \right) E_p = \left( \frac{5000}{50} \right) (4) = 400 \text{ volt}$$



$$I = \frac{1}{4} \text{ A}$$

Power in  $R_1$


$$V_A + 3 - \frac{7}{2} \times 2 - V_B = 0 \quad P_1 = I^2 R = \left( \frac{7}{2} \right)^2 \times 2$$

$$\Rightarrow V_A - V_B = 4 \text{ V}$$

$$P = 24.5 \text{ W}$$

$$(ii) i_0 = i_0 (1 - e^{-t/\tau})$$

$$i_0 = \frac{3}{2+3} = 0.6 \text{ A}$$

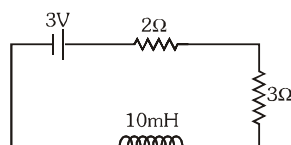

$$\tau = \frac{L}{R_{\text{eq}}} = \frac{10 \times 10^{-3}}{5} = 2 \times 10^{-3} \text{ sec}$$

$$(A) i_0 = 0.6 \text{ A}$$

$$(B) \frac{i_0}{2} = i_0 (1 - e^{-t/\tau}) \Rightarrow \frac{1}{2} = 1 - e^{-t/\tau}$$

$$\Rightarrow e^{-t/\tau} = \frac{1}{2} \Rightarrow t/\tau = \ln 2$$

$$t = \tau \ln 2 \Rightarrow t = 2 \times 10^{-3} \times 0.693$$

$$\Rightarrow t = 1.38 \times 10^{-3} \text{ sec}$$

Energy stored in L :


$$H = \frac{1}{2} Li^2 = \frac{1}{2} \times 10 \times 10^{-3} \left( \frac{0.6}{2} \right)^2$$

$$\Rightarrow H = 4.5 \times 10^{-4} \text{ J}$$

11. Here  $V_{L_1} = V_{L_2}$

$$\Rightarrow L_1 \frac{di_1}{dt} = L_2 \frac{di_2}{dt}$$

$$\Rightarrow L_1 i_1 = L_2 i_2$$

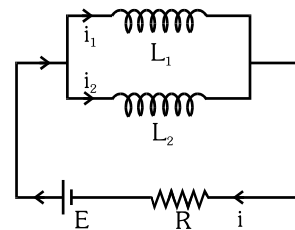


$$\text{But } i_1 + i_2 = \frac{E}{R} = i \Rightarrow i_1 = \left( \frac{L_2}{L_1 + L_2} \right) \left( \frac{E}{R} \right)$$

$$\text{Hence (i) Current in } L_1 = \left( \frac{L_2}{L_1 + L_2} \right) \left( \frac{E}{R} \right)$$

$$(ii) \text{ Current in } R = \frac{E}{R}$$

12. (i) At  $t=0$

L act as open circuit

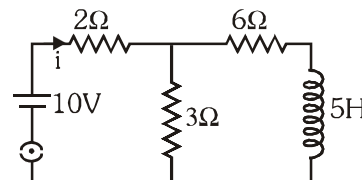

$$\text{So } i = \frac{10}{2+3} \Rightarrow i = 2 \text{ A}$$

- (ii) After some time

L act as short circuit

$$i = \frac{10}{2 + \frac{6 \times 3}{6+3}} = \frac{10}{2+2} \Rightarrow i = 2.5 \text{ A}$$

13. (i) After 100 ms wave is repeated so time

$$\text{period is } T = 100 \text{ ms. } \Rightarrow f = \frac{1}{T} = 10 \text{ Hz}$$

- (ii) Average value = Area/time period

$$= \frac{(1/2) \times 100 \times 10}{(100)} = 5 \text{ volt}$$

$$14. I_{\text{rms}} = \sqrt{\langle (I_1 \cos \omega t + I_2 \sin \omega t)^2 \rangle}$$

$$= \sqrt{I_1^2 \langle \cos^2 \omega t \rangle + I_2^2 \langle \sin^2 \omega t \rangle + 2I_1 I_2 \langle \sin \omega t \cos \omega t \rangle}$$

$$= \sqrt{I_1^2 \left( \frac{1}{2} \right) + I_2^2 \left( \frac{1}{2} \right) + 2I_1 I_2 (0)} = \sqrt{\frac{I_1^2 + I_2^2}{2}}$$

$$15. (i) T = \frac{2\pi}{\omega} = \frac{2 \times 3.14}{628} = \frac{1}{100} = 0.01 \text{ s}$$

- (ii) 60 (30 - C - 30)

16. (i) Impedance

$$Z = \frac{V_0}{I_0} = \frac{110}{5} = 22 \Omega \quad (ii)$$

Power factor

$$= \cos \phi = \cos \left( \frac{\pi}{3} \right) = \frac{1}{2} \text{ (lagging)}$$

- 17.
- $R = 100 \, \Omega$
- ;
- $f = 1000 \text{ Hz}$
- ,
- $\phi = 45$

$$\tan \phi = \frac{X_L}{R} \Rightarrow X_L = R \tan \phi = 100 \quad 1 = 100 \, \Omega$$

$$\therefore X_L = 2\pi fL = 100 \quad \therefore L = \frac{100}{2 \times 3.14 \times 1000}$$

$$= 0.0159 \text{ H} = 15.9 \text{ mH}$$

18. (i) X is resistor and Y is a capacitor
- 
- (ii) Since the current in the two devices is the same (0.5A at 220 volt)

When R and C are in series across the same voltage then

$$R = X_C = \frac{220}{0.5} = 440 \, \Omega \Rightarrow I_{\text{rms}} = \frac{V_{\text{rms}}}{\sqrt{R^2 + X_C^2}}$$

$$= \frac{220}{\sqrt{(440)^2 + (440)^2}} = \frac{220}{440\sqrt{2}} = 0.35 \text{ A}$$

19. (i) resistor (ii) inductor

20. (i) At resonance condition
- $X_L = X_C$

$$\Rightarrow \omega_0 L = \frac{1}{\omega_0 C} \Rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$$

$$(ii) \therefore \cos \phi = \frac{R}{Z} = \frac{R}{R} = 1$$

$$\therefore \phi = 0$$

No, It is always zero.

21. (i) Impedance of the circuit

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{(4)^2 + (7-4)^2} = 5 \, \Omega$$

current flow in ckt.

$$I_{\text{rms}} = \frac{V_{\text{rms}}}{Z} = \frac{25/\sqrt{2}}{5} = \frac{5}{\sqrt{2}} \text{ A}$$

 $\therefore$  Heat developed

$$= I_{\text{rms}}^2 R t = \left( \frac{5}{\sqrt{2}} \right)^2 \times 4 \times 80 = 4000 \text{ joule}$$

OR

$$H = Pt = (VI \cos \phi) t = \left( \frac{25}{\sqrt{2}} \cdot \frac{5}{\sqrt{2}} \times \frac{4}{5} \right) 10 = 4000$$

$$J \left( \text{Use } \cos \phi = \frac{R}{Z} \right)$$

$$(ii) \text{Wattless current} = I_{\text{rms}} \sin \phi$$

$$= \frac{5}{\sqrt{2}} \quad \frac{3}{5} = 2.12 \text{ A} \left( \because \sin \phi = \frac{X_L - X_C}{Z} = \frac{3}{5} \right)$$

22. Impedance of circuit

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{(45)^2 + (4-4)^2} = 45 \, \Omega$$

$$\text{Total current in circuit } I = \frac{V}{Z} = \frac{90}{45} = 2 \text{ A}$$

(Reading of ammeter)

Voltmeter connect across L and C

so reading of voltmeter =  $V_L - V_C$ 

$$\text{Now } X_L = X_C \Rightarrow V_L = V_C$$

So reading of voltmeter = 0

23. Power dissipation

$$= V I \cos \phi = V \cdot \frac{V}{Z} \cdot \frac{R}{Z} = \frac{V^2 R}{Z^2} \quad \dots (1)$$

$$\left[ \because \cos \phi = \frac{R}{Z}, I = \frac{V}{Z} \right]$$

$$V = 100 \text{ V}, R = 10 \, \Omega, Z = \sqrt{R^2 + (X_L)^2} = 10\sqrt{2} \, \Omega$$

$$\left( \begin{array}{l} X_L = \omega L = 2\pi \times 50 \times \frac{1}{10\pi} \\ X_L = 10 \, \Omega \end{array} \right)$$

Put all these value in eq (1)

$$P_{\text{loss}} = \frac{100 \times 100 \times 10}{(10\sqrt{2})^2} = 500 \text{ watt}$$


24. Mutual inductance

$$M = \frac{\phi_s}{I_p} = \frac{B(\pi r^2)}{I} = \frac{\sqrt{3}\mu_0 I (\pi r^2)}{\pi a I} = \frac{\sqrt{3}\mu_0 r^2}{a}$$

$$25. \vec{E} = \vec{B} \cdot \vec{L} \times \vec{v} = -B_0 \hat{k} \cdot \hat{\lambda} \hat{i} \times (v_x \hat{i} + v_y \hat{j})$$

$$= -B_0 \hat{k} \cdot \lambda v_y \hat{k} = -\lambda v_y B_0$$

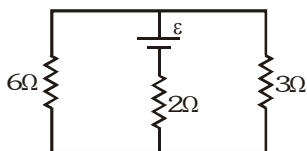
$$26. R_{\text{eff}} = \frac{3 \times 6}{3+6} + 2 = 4\Omega$$



$$\therefore I = \frac{\varepsilon}{R_{\text{eff}}} = \frac{BLv}{R_{\text{eff}}} = \frac{2 \times 1 \times 2}{4} = 1\text{A}$$

$$\therefore F = ILB = 1 \times 1 \times 2 = 2\text{N}$$
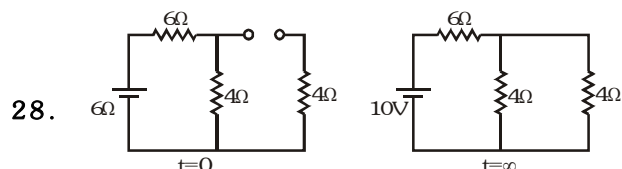
$$27. mg = ILB = \left( \frac{BLv_T}{R} \right) LB \Rightarrow v_T = \frac{mgR}{L^2 B^2}$$



28.

$$I_1 = \frac{10}{6+4} = 1\text{A}$$

$$I_2 = \frac{10}{6+2} = \frac{5}{4}\text{A}$$

$$\therefore \frac{I_1}{I_2} = 0.8$$

$$29. I = \frac{E}{R} [1 - e^{-t/\tau}] \left( \tau = \frac{L}{R} \right)$$

$\therefore$  Charge passed through the battery

$$= \int Idt = \frac{E}{R} \int_0^\tau (1 - e^{-t/\tau}) dt = \frac{E}{R} \left[ t + \tau e^{-t/\tau} \right]_0^\tau$$

$$= \frac{E}{R} [(\tau + \tau/e) - (0 + \tau)] = \frac{EL}{eR^2}$$

$$30. \left( \frac{1}{2} Li^2 \right) = \frac{1}{4} \left( \frac{1}{2} Li^2 \right) \Rightarrow i = \frac{I}{2}$$


$$\text{where } i = \frac{I}{2} = Ie^{-t/\tau} \Rightarrow \tau = \frac{L}{R} \Rightarrow \frac{t}{\tau} = \ln 2$$

$$\therefore \text{Charge flown} = \int_0^{t=\tau \ln 2} idt = \int_0^{\tau \ln 2} (Ie^{-t/\tau}) dt$$

$$= I\tau \left[ -e^{-t/\tau} \right]_0^{\tau \ln 2} = I\tau \left( \frac{1}{2} \right) = \frac{IL}{2R}$$

## EXERCISE -IV (B)

1.

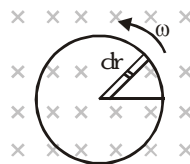


$$(i) e = \int de = \int_0^r B\omega dr = \frac{1}{2} B\omega r^2$$

$$(ii) I = I_0 \left( 1 - e^{-\frac{Rt}{L}} \right) = \frac{B\omega r^2}{2R} \left( 1 - e^{-\frac{Rt}{L}} \right)$$

Now torque required for power losses

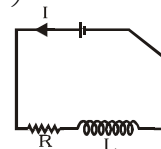
$$\left( P = I^2 R = \frac{B^2 r^4 \omega^2}{4R} \right)$$



$$\tau_1 = \frac{P}{\omega} = \frac{B^2 r^4 \omega^2}{4R\omega} = \frac{B^2 r^4 \omega}{4R}$$

Torque required to move the rod in circular motion against gravitational field
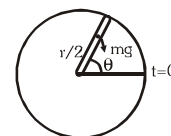
$$\tau_2 (mg) \left( \frac{r}{2} \cos \theta \right) = \frac{1}{2} mgr \cos \omega t$$




The total torque

$$\tau = \tau_1 + \tau_2 = \frac{B^2 r^4 \omega}{4R} + \frac{1}{2} mgr \cos \omega t$$

Direction of torque : clockwise

$$2. I_0 = \frac{10}{2} = 5$$

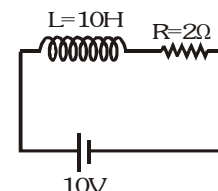

$$\text{Magnetic energy} = \frac{1}{2} Li^2$$

The current in the circuit for one fourth of magnetic

$$\text{energy } I = \frac{I_0}{2}$$


$$\text{But } I = I_0 \left( 1 - e^{-\frac{Rt}{L}} \right) \Rightarrow \frac{I_0}{2} = I_0 \left( 1 - e^{-\frac{Rt}{L}} \right)$$

$$\Rightarrow e^{-t/5} = \frac{1}{2} \Rightarrow e^{t/5} = 2 \Rightarrow \frac{t}{5} = \ln 2$$

$$\Rightarrow t = 5 \ln 2 = 5 \times 0.693 = 3.47 \text{ s}$$

3.

Refer to figure.

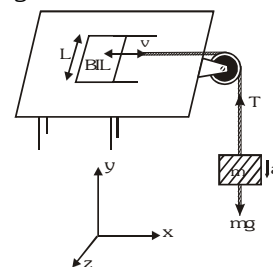

Let  $v$  be the velocity of the rod along the positive  $x$ -direction at an instant of time and let the magnetic field  $B$  act perpendicular to the table along the positive  $y$ -direction.

The emf induced in the rod is  $e = BLv$ .

Therefore, the induced current is

$$I = \frac{e}{R} = \frac{BLv}{R}$$

The rod of length  $L$  carrying a current  $I$  in magnetic field will experience a force  $F = BIL$  ... (2)

along the negative  $x$ -direction. Since the rod is massless, this force will also be equal to the tension  $T$  in the string acting along the positive  $x$ -direction, i.e.

$$T = F = BIL$$

Let  $a$  be the acceleration of mass  $m$  moving in the downward direction, then  $ma = \text{net force acting on}$

$$m = mg - T = mg - F \text{ or } a = g - \frac{F}{m} \dots (3)$$

Using (1), (2) and (3), we have

$$a = g - \frac{B^2 L^2 v}{mR} = g - \frac{B^2 L^2 v}{mR} \dots (4)$$

(i) The rod will acquire terminal velocity  $v_t$  when  $a = 0$ .

Putting  $a = 0$  and  $v = v_t$  in eq. (4)

$$\text{we have } 0 = g - \frac{B^2 L^2 v_t}{mR} \text{ or } v_t = \frac{mgR}{B^2 L^2}$$


(ii) When the velocity of the rod is half the terminal

$$\text{velocity i.e. when } v = \frac{v_t}{2} = \frac{mgR}{2B^2 L^2}$$

then from equation (4), we have

$$a = g - \frac{B^2 L^2 v_t / 2}{mR} = g - \frac{B^2 L^2}{2mR} \cdot \frac{mgR}{B^2 L^2} = g - \frac{g}{2} = \frac{g}{2}$$

4. Refer to figure

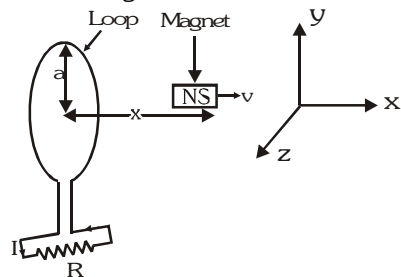

The magnetic field at distance  $x$  on the axis of a magnetic of length  $2\ell$  and dipole moment  $M$  is given by

$$B = \frac{\mu_0}{2\pi} \frac{Mx}{(x^2 - \ell^2)^2}$$

$$\therefore x \gg \ell, \text{ we have } B = \frac{\mu_0 M}{2\pi x^3}$$

Due to  $B$ , the flux through the loop is

$$\phi = BA = B(\pi a^2) = \frac{\mu_0 M}{2\pi x^3} \pi a^2 = \frac{\mu_0 M a^2}{2x^2}$$

Induced emf in the loop is

$$e = - \frac{d\phi}{dt} = - \frac{dx}{dt} \frac{d\phi}{dx} = v \frac{d\phi}{dx} \\ = \frac{\mu_0 M a^2 v}{2} \frac{d}{dx} \left( \frac{1}{x^2} \right) = \frac{3}{2} \frac{\mu_0 M a^2 v}{x^3}$$


$\therefore$  Induced current in the loop is

$$I = \frac{e}{R} = \frac{3}{2} \frac{\mu_0 M a^2 v}{x^3 R}$$

Magnetic moment of the loop is

$$M_0 = I \cdot \text{area enclosed by the loop} = I(\pi a^2)$$
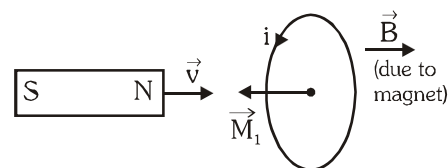
$$= \frac{3}{2} \frac{\mu_0 M a^2 v}{x^3 R}$$



Potential energy

$$U = -\vec{M} \cdot \vec{B} = -MB \cos 180^\circ \Rightarrow U = M'B$$


$$= \frac{3}{2} \frac{\mu_0 \pi M a^2 v}{R x^3} \left( \frac{\mu_0 M}{2\pi x^3} \right)$$

$$U = \frac{3}{4} \frac{\mu_0 M^2 a^2 v}{R} \times \frac{1}{x^7}$$

$$F = - \frac{dU}{dx} \Rightarrow F = \frac{21}{4} \frac{\mu_0 M^2 a^4 v}{R x^8}$$

This force is caused by the moving magnet. From Lenz's law, this force opposes the motion of the magnet.

5.

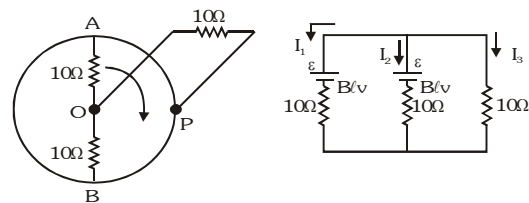

$$\varepsilon = \frac{B\omega L^2}{2} = \frac{50 \times 20 \times 0.1 \times 0.1}{2} = 5V$$

For the circuit  $I_1 + I_2 + I_3 = 0$

$$\Rightarrow \frac{V-5}{10} + \frac{V-5}{10} + \frac{V}{10} = 0 \Rightarrow V = \frac{10}{3}$$

$$\therefore I_3 = \frac{V}{10} = \frac{1}{3} A$$

6. Initial current through L for switch in position =  $\frac{\varepsilon}{R_1}$

$$\therefore \text{Energy stored in inductor} = \frac{1}{2} L \left( \frac{\varepsilon}{R_1} \right)^2 = \frac{L\varepsilon^2}{2R_1^2}$$

$$\therefore \text{Heat developed across } R_2 = \frac{L\varepsilon^2}{2R_1^2}$$

7.  $\varepsilon = E2\pi r = \pi r^2 \frac{dB}{dt} \Rightarrow E = \frac{r}{2} k$

$$\therefore \text{For an electron } a = \frac{f}{m} = \frac{eE}{m} = \frac{erK}{2m}$$

8.  $\phi = MI \Rightarrow \varepsilon = \left| -\frac{d\phi}{dt} \right| = M(2kt)$

$$\therefore \Delta Q = \int_0^T \frac{\varepsilon}{R} dt = \frac{kMT^2}{R}$$

9.  $E2\pi R = \pi R^2 \frac{dB}{dt} \Rightarrow E = \frac{R}{2} \frac{d(0.2t)}{dt} = \frac{R}{2} (0.2) = \frac{R}{10}$

$\therefore$  Torque on coil

$$= qER = q \left( \frac{R}{10} \right) R = I\alpha = mR^2\alpha$$

$\Rightarrow$  Angular velocity attained

$$\omega = \alpha\Delta T = \left( \frac{qER}{mR^2} \right) \Delta t = 40 \text{ rad/sec}$$

10. For LC circuit  $\frac{q}{c} + \frac{Ldi}{dt} = 0$

$$\Rightarrow q = Q_0 \sin(\omega t + \phi) \left( \omega = \frac{1}{\sqrt{LC}} \right)$$

$$\text{At } t=0, q = Q_0 \Rightarrow Q_0 = Q_0 \sin \phi \Rightarrow \phi = \pi/2$$

$$\therefore q = Q_0 \sin \left( \frac{t}{\sqrt{LC}} + \frac{\pi}{2} \right)$$

11.  $\phi = BA = (Kt - C)(\pi a^2)$


$$\text{Charge } q = \frac{\Delta\phi}{R} = \frac{\phi_2 - \phi_1}{R}$$

$$\text{At } t=0; \phi_1 = -C(\pi a^2)$$

$$\text{At } t = \frac{C}{k} \phi_2 = 0$$

$$\text{So } q = 0 - \left( \frac{-C\pi a^2}{R} \right) \Rightarrow q = \frac{C\pi a^2}{R}$$

13.  $B = 0.042 - 0.87 t$

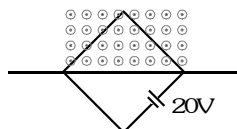

(ii) B is decreasing with B so induced current will try to increase (B) (Lenz's law). So direction of current anticlockwise


(i) For upper half area

$$e = -\frac{AdB}{dt} = - \left( \frac{2 \times 2}{2} \right) (-0.87)$$


$$\Rightarrow e = 1.74 \text{ Volt}$$

Total emf in circuit
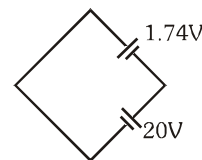
$$E = 1.74 + 20 \Rightarrow E = 21.74 \text{ volts}$$



14.  $e = Bv\ell$ ,  $de = (dB)vdx$

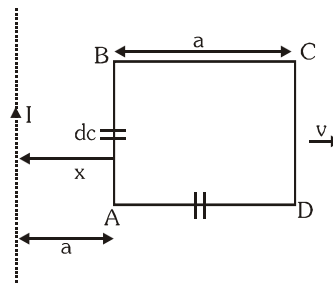

induced current will be clockwise

$$\text{in AB : } e_1 = \int_0^{2a} \frac{\mu_0 I}{2\pi x} v dx \Rightarrow e_1 = \frac{\mu_0 I v}{2\pi} \ln 2$$

$$\text{in CD : } e_2 = \int_{2a}^{3a} \frac{\mu_0 I}{2\pi x} v dx \Rightarrow e_2 = \frac{\mu_0 I v}{2\pi} \ln \frac{3}{2}$$

$$\text{So net } e = e_2 - e_1 = \frac{\mu_0 I v}{2\pi} \ln \frac{3}{4} \Rightarrow i = \frac{e}{R} = \frac{\mu_0 I v}{2\pi R} \ln \frac{3}{4}$$

$$\text{Force } F = i\ell B, dF = i(dx) dB$$


$$\text{Work done } dW = dF \cdot x$$

$$W = \int_0^{2a} i(dx) \left( \frac{\mu_0 I}{2\pi x} \right) \cdot x$$

$$\Rightarrow W = \frac{i\mu_0 I}{2\pi} \int_0^{2a} dx = \frac{i\mu_0 I}{2\pi} (2a - a)$$

$$\Rightarrow W = \frac{\mu_0 I^2 Va}{4\pi^2 R} \ln \frac{3}{4}$$

- 16.

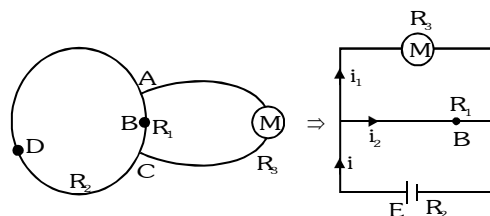


$$i = \frac{E}{\frac{R_1 R_3}{R_1 + R_3} + R_2} = \frac{E(R_1 + R_3)}{R_1 R_2 + R_2 R_3 + R_1 R_3}$$

$$i = \frac{R_1}{R_1 + R_3} = \frac{ER_1}{R_1 R_2 + R_2 R_3 + R_1 R_3}$$



17.

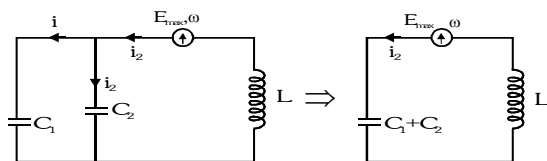

$$i_{\max} = \left( \frac{E_{\max}}{\omega L - \frac{1}{\omega(C_1 + C_2)}} \right) = \frac{E_{\max}}{X_L - X_C}$$

$$\Rightarrow (i_1)_{\max} = \frac{C_1}{C_1 + C_2} i_{\max}$$

$$\Rightarrow (i_1)_{\max} = \frac{C_1 I_{\max}}{(C_1 + C_2) \left( \omega L - \frac{1}{\omega(C_1 + C_2)} \right)}$$

$$\text{and } (i_2)_{\max} = \frac{C_2}{C_1 + C_2} i_{\max}$$

$$(i_2)_{\max} = \frac{C_2 E_{\max}}{(C_1 + C_2) \left( \omega L - \frac{1}{\omega(C_1 + C_2)} \right)}$$

18.  $i = 3 + 5t$ ,  $R = 4\Omega$ ,  $L = 6H$

$$\because E = iR + L \frac{di}{dt} = (3+5t) 4 + 6(5)$$

$$E = 42 + 20t$$

19.(i) Let  $v$  be the velocity of the rod MN at an instant of time  $t$  when it is at a distance  $x$  from R. Then, the induced emf at that instant is  $e = Bvd$ . Since  $\lambda$  is the resistance per unit length of each wire, the total resistance in series with R at that instant is

$$\lambda x + \lambda x = 2\lambda x.$$

Thus the total resistance of the circuit at time  $t$  is  $R + 2\lambda x$ .

Hence the current in the circuit is

$$I = \frac{\text{induced emf}}{\text{total resistance}} = \frac{Bvd}{(R + 2\lambda x)} = \text{constant (given)}$$

$$\therefore v = \frac{I(R + 2\lambda x)}{Bd} \dots (1)$$

The magnetic force acting on the rod is  $F_m = BId$  directed to the left.

The net force acting on the rod is

$$F_{\text{net}} = F - F_m = F - BId \dots (2)$$

$F_{\text{net}}$  is the force experienced by the rod MN at time  $t$  when its velocity is  $v$  at a distance  $x$  from R.

From Newton's law

$$F_{\text{net}} = ma = m \frac{dv}{dt} = m \frac{dv}{dx} \frac{dx}{dt}$$

Now  $\frac{dx}{dt} = v$ . Using (1), we have

$$F_{\text{net}} = mv \frac{d}{dt} \left\{ \frac{I(R + 2\lambda x)}{Bd} \right\} = \frac{2mv\lambda I}{Bd}$$

( $\because$  I, R, B and d are constants)

$$= \frac{2m\lambda I^2}{B^2 d^2} (R + 2\lambda x) \text{ [Use equation (1)]}$$

Using this in equation (2), we get

$$F = BId + \frac{2m\lambda I^2}{B^2 d^2} (R + 2\lambda x) \dots (3)$$

(ii) Work done in time  $dt = Fdx$ .

Therefore, work done per second i.e., power is

$$P = \frac{d}{dt} (Fdx) = \frac{Fdx}{dt} = Fv$$

Using Equation (1), we have

$$P = \frac{FI(R + 2\lambda x)}{Bd}$$

Heat produced per second is



$$Q = I^2 (R + 2\lambda x)$$

$$\therefore \text{Ratio } \frac{Q}{P} = \frac{I^2 (R + 2\lambda x) Bd}{FI(R + 2\lambda x)} = \frac{IBd}{F} \dots (4)$$

Using (3) in (4), we get

$$\frac{Q}{P} = \frac{B^3 d^3}{B^3 d^3 + 2m\lambda I(R + 2\lambda x)}$$

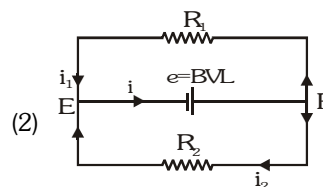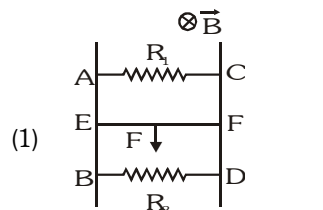20. Let the magnetic field be perpendicular to the plane of rails and inwards  $\otimes$ . If  $V$  be the terminal velocity of the rails, then potential difference across E and F would be  $BVL$  with E at lower potential and F at higher potential. The equivalent circuit is shown in figure (2). In figure (2).



$$i_1 = \frac{e}{R_1} \dots (1)$$

$$i_2 = \frac{e}{R_2} \dots (2)$$

Power dissipated in  $R_1$  is 0.76 watt

Therefore (इसलिए)  $e i_1 = 0.76$  watt  $\dots (3)$


Similarly (इसी प्रकार)  $e i_2 = 1.2$  watt  $\dots (4)$

Now the total current in bar EF is

$i = i_1 + i_2$  (From E to F)  $\dots (5)$

Under equilibrium condition, magnetic force ( $F_m$ ) on bar EF = weight ( $F_g$ ) of bar EF

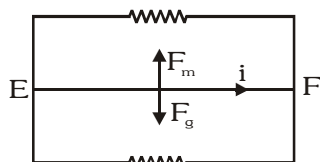i.e.,  $F_m = F_g$  or  $iLB = mg \dots (6)$



From equation (6)

$$i = \frac{mg}{LB} = \frac{0.2(9.8)}{(1.0)(0.6)} \text{ A or } i = 3.27 \text{ A}$$

Multiplying equation (5) by  $e$ , we get

$e i = e i_1 + e i_2 = (0.075 + 1.2)$  watt  
(From equation 3 and 4) = 1.96 watt

$$e = \frac{1.96}{i} \text{ volt} = \frac{1.96}{3.27} \text{ V or } e = 0.6 \text{ V}$$

But since  $e = BVL$

$$V = \frac{e}{BL} = \frac{(0.6)}{(0.6)(1.0)} \text{ m/s} = 1.0 \text{ m/s}$$

Hence, terminal velocity of bar is 1.0 m/s.

Power in  $R_1$  is 0.76 watt


$$\therefore 0.76 = \frac{e^2}{R_1} \therefore R_1 = \frac{e^2}{0.76} = \frac{(0.6)^2}{0.76} \Omega = 0.47 \Omega$$

$$R_1 = 0.47 \Omega$$

$$\text{Similarly } R_2 = \frac{e^2}{1.2} = \frac{(0.6)^2}{1.2} \Omega = 0.3 \Omega$$

$$R_2 = 0.3 \Omega$$

21. Refer to figure

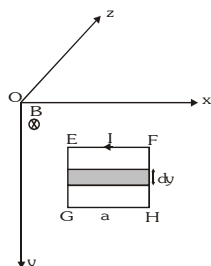

- (i) Consider a small element of the loop of width  $dy$  and side  $a$ . The area of the element  $dA = a dy$ . Since the area vector and the magnetic field vector point in the same direction, i.e. the angle  $\theta$  between the normal to the plane of the loop and the magnetic

field is zero, the magnetic flux through the element

$$d\phi = BdA \cos \theta = BdA \cos 0^\circ = BdA$$

The total magnetic flux linked with the loop is

$$\phi = \int BdA \therefore B = B_0 \left( \frac{y}{a} \right) \tilde{k}$$

depends upon  $y$ , we have

$$\phi = \int_y^{y+a} B_0 \left( \frac{y}{a} \right) a dy = B_0 \int_y^{y+a} y dy = \frac{B_0}{2}$$

$$\left[ y^2 \right]_y^{y+a} = \frac{B_0}{2} [(y+a)^2 - y^2] \dots (1)$$


$\therefore$  Induced emf is

$$e = - \frac{d\phi}{dt} = - \frac{B_0}{2} \frac{d}{dt} [(y+a)^2 - y^2] = - \frac{B_0}{2}$$

$$\left[ 2(y+a) \frac{dy}{dt} - 2y \frac{dy}{dt} \right] = - B_0 a \frac{dy}{dt}$$

$$\text{The induced current is } I = \frac{|e|}{R} = \frac{B_0 a}{R} \frac{dy}{dt} \dots (2)$$

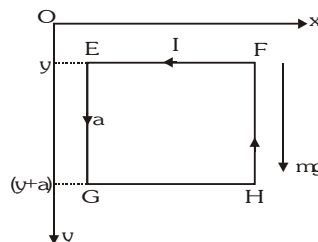Since the magnetic field  $B$  points in the positive  $z$ -direction, it follows from Lenz's law that the direction of the induced current will be along the negative  $z$ -axis. Thus the current in the loop will flow in the counterclockwise direction as shown in figure.



- (ii) The Lorentz force acting on a current element  $I d\ell$  in magnetic field  $B$  is given by

$$F = I \oint_L (d\ell \times B)$$

Now, the forces acting on sides EG and FH of the loop are equal and opposite. Hence they cancel each other. The forces acting on sides EF and GH are in opposite directions but their magnitudes are different since  $B$  depends upon  $y$ . Thus, force acting on side

$$\text{EF is } F_{EF} = I \left[ (a\tilde{i}) \times \left( \frac{B_0 y}{a} \tilde{k} \right) \right] = IB_0 y \tilde{j}$$

Similarly, force acting on side GH is

$$F_{GH} = I \left[ (a\tilde{i}) \times \left\{ \frac{B_0 (y+a)}{a} \right\} \tilde{k} \right] = -IB_0 (y+a) \tilde{j}$$

Therefore, the net force acting on the loop is

$$F_{\text{net}} = F_{EF} + F_{GH} = IB_0 y \tilde{j} - IB_0 (y+a) \tilde{j} = -IB_0 a \tilde{j}$$

Substituting the expression for  $I$  from equation (2),

we get

$$F_{\text{net}} = - \left( \frac{B_0^2 a^2}{R} \right) \frac{dy}{dt} \hat{j}$$

The negative sign  $(-\hat{j})$  indicates that the force acts along the negative y-direction.

- (iii) As force  $F_{\text{net}}$  is directed along the negative y-axis and the gravitational force  $mg$  is along the positive y-direction, the total force on the loop in the downward (positive y) direction is

$$F = mg - \left( \frac{B_0^2 a^2}{R} \right) \frac{dy}{dt}$$

where  $\frac{dy}{dt} = v$ , the speed with which the loop is falling downwards. From newton's second law, the equation of motion of the loop is

$$F = \text{mass} \times \text{acceleration} \quad \text{or} \quad F = m \frac{dv}{dt}$$

$$\therefore m \frac{dv}{dt} = mg - \left( \frac{B_0^2 a^2}{R} \right) v$$

$$\text{or} \quad \frac{dv}{dt} = g - \left( \frac{B_0^2 a^2}{mR} \right) v \quad \text{or} \quad \frac{dv}{dt} = g - kv \quad \dots (3)$$

$$\text{where } k = \frac{B_0^2 a^2}{mR}$$

Rearranging expression (3), we have  $\frac{dv}{(g - kv)} = dt$

Integrating, we have

$$\int_0^v \frac{dv}{(g - kv)} = \int_0^t dt \quad \text{or} \quad -\frac{1}{k} \log_e \left[ \frac{(g - kv)}{g} \right] = t$$

which gives

$$v = \frac{g}{k} (1 - e^{-kt}) = \frac{gmR}{B_0^2 a^2} \left[ 1 - \exp \left( -\frac{B_0^2 a^2 t}{mR} \right) \right]$$

This is the required expression for the speed  $v$  of the loop as a function of time  $t$ . When the loop acquires terminal velocity  $v_0$  no force acts on it. Hence its acceleration  $dv/dt$  is zero.

Using this in equation (3), we have

$$0 = g - kv_t \quad \text{or} \quad v_t = \frac{g}{k} = \frac{mgR}{B_0^2 a^2}$$


22. flux  $\phi = BA$ ;  $d\phi = (dB)(dA) \Rightarrow d\phi = \left( \frac{\mu_0 I}{2\pi x} \right) (\ell dx)$

$$\phi = \int_a^{a+b} d\phi = \frac{\mu_0 I \ell}{2\pi} \int_a^{a+b} \frac{1}{x} dx$$

$$\frac{\mu_0 I \ell}{2\pi} (\ln x)_a^{a+b} \Rightarrow \phi = \frac{\mu_0 I \ell}{2\pi} \ln \left( \frac{a+b}{a} \right)$$

## EXERCISE -V(A)


1.

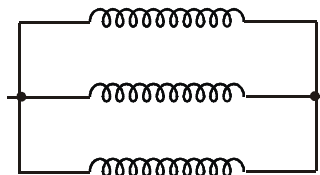


In parallel  $\frac{1}{L} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}$

$$\frac{1}{L} = \frac{1}{3} + \frac{1}{3} + \frac{1}{3} = \frac{3}{3} = 1 \quad \text{as } L = 1H$$

2.

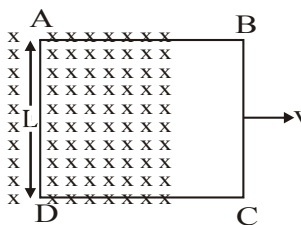

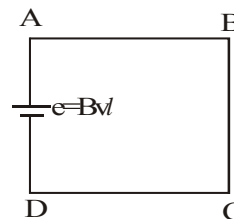The equivalent circuit of the conductor will be



4. The core of transformer is laminated so as to reduce the energy loss due to eddy currents.

6.

$$I_1 = 2A$$

$$I_2 = -2A$$

$$t = 0.05, \quad e = 8V$$

$$e = \frac{-L di}{dt} = -L \left[ \frac{-2A - 2A}{0.05} \right]$$

$$8 = L \left[ \frac{4}{0.05} \right]$$

$$L = 2 \times 0.05 = 0.1 H$$

7.

Number of turns =  $n$   
 Resistance of coil =  $R\Omega$   
 Resistance of galvanometer =  $4R\Omega$


$$\text{Induced current} = \frac{e}{R}$$

$$= - \left[ \frac{\phi_2 - \phi_1}{t} \right] \frac{1}{\text{Resistance of circuit}}$$

$$= - \left[ \frac{nW_2 - nW_1}{t} \right] \frac{1}{5R}$$

$$= -n \left[ \frac{W_2 - W_1}{5Rt} \right]$$

8.

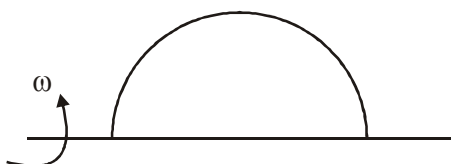

The flux associated with coil =  $NBA \cos \omega t$

$$\phi = B \frac{\pi r^2}{2} \cos \omega t$$

$$e = \frac{-d\phi}{dt} = \frac{B\pi r^2 \omega}{2} \sin \omega t$$

$$P_{\text{inst.}} = \frac{e^2}{R} = \left( \frac{B\pi r^2 \omega}{2} \right) \frac{\sin^2 \omega t}{R}$$

$$P_{\text{av}} = \frac{\int P dt}{\int dt} = \frac{B^2 \pi^2 r^4 \omega^2}{4R} \frac{\int \sin^2 \omega t dt}{\int dt}$$

$$\int_0^T \sin^2 \omega t dt = \frac{1}{2} T$$

$$\text{Hence } P_{\text{av}} = \frac{B^2 \pi^2 r^4 \omega^2}{4R} \frac{1}{2}$$

$$P_{\text{av}} = \frac{B^2 \pi^2 r^4 \omega^2}{8R}$$

$$P_{\text{av}} = \frac{(B\pi r^2 \omega)^2}{8R}$$

9. The emf developed across the ends of the pivoted

$$\text{rod is } e = \frac{B\ell^2 \omega}{2}$$

$$\omega = 5 \frac{\text{rad}}{\text{sec}}, B = 0.2 \times 10^{-4} \text{ T}, L = 1 \text{ m}$$

$$e = \frac{0.2 \times 10^{-4} \times 1^2 \times 5}{2} = 5 \times 10^{-5} = 50 \mu\text{V}$$


$$10. I_{\text{steady}} = \frac{V}{R} = \frac{2}{2} = 1 \text{ A}; I = I_0 \left( 1 - e^{-\frac{R}{L}t} \right)$$

$$\frac{R}{L} = \frac{2}{300 \times 10^{-3}} = \frac{2000}{300}$$

$$\frac{I_0}{2} = I_0 \left( 1 - e^{-\frac{R}{L}t} \right)$$

$$\frac{1}{2} = 1 - e^{-\frac{R}{L}t} \Rightarrow t = \frac{\ell n 2}{L/R} \approx 0.1 \text{ s}$$

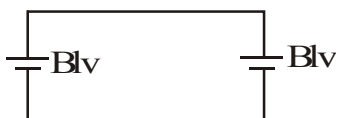11. The vertical arm of the both tubes will become a battery of emf  $Blv$ .



The emf induced in the circuit is  $2 Blv$ .


$$12. \phi = 10t^2 - 50t + 250$$

$$\frac{d\phi}{dt} = 20t - 50$$

$$e = \frac{-d\phi}{dt} = 50 - 20t$$

$$e_{(t=3)} = 50 - 20 \times 3 = -10 \text{ V}$$
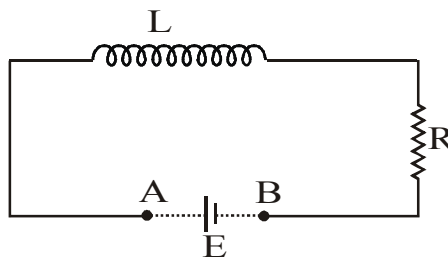
$$13. L = 100 \text{ mH}; R = 100 \Omega; E = 100 \text{ V}$$




Long time after, current in the circuit is

$$I_0 = \frac{E}{R} = 1 \text{ A}$$

On short circuiting  $I = I_0 e^{-\frac{R}{L}t}$

$$I = 1 e^{-\frac{100}{100 \times 10^{-3}} \times 10^{-3}}$$
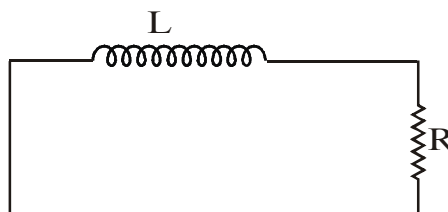
$$I = \left( \frac{1}{e} \right) \text{ A}$$



14. RMS value of electric field =  $720 \text{ N/C}$

Peak value of electric field =  $\sqrt{2} \times 720 \text{ N/C}$

the average total energy density of electromagnetic

$$\text{wave} = \frac{1}{2} \epsilon_0 E_0^2; u_{\text{av}} = \frac{1}{2} \epsilon_0 E_0^2$$

On solving we get

$$u_{\text{av}} = 4.58 \times 10^{-6} \text{ J/m}^3$$

15. Inductance of the coil  $L = 10 \text{ H}$

Resistance of the coil  $R = 5 \Omega$

As R-L is connected across battery, hence nature of current that will flow through the circuit will be transient current, i.e.,  $I = I_0 (1 - e^{-t/\tau})$

$$\text{where } \tau = \frac{L}{R} = \frac{10}{5} = 2 \text{ s and } I_0 = \frac{V}{R} = \frac{5}{5} = 1 \text{ A}$$

$$\text{hence } I = 1(1 - e^{-2/2}); I = (1 - e^{-1}) \text{ A}$$

16.  $M = \frac{\mu_0 N_1 N_2 A}{\ell} = 2.4\pi \times 10^{-4} \text{ H}$

17. Equivalent resistance across L (by short circuiting battery) =  $R_{eq} = 2\Omega$

then current through L  $i = i_0(1 - e^{-Rt/L})$

where  $R = 2\Omega$ ,  $L = \frac{4}{10} \text{ H}$ ,  $i_0 = \frac{E}{R} = \frac{12}{2} = 6 \text{ A}$


$i = 6(1 - e^{-5t}) \dots (i)$

$\therefore$  p.d. across L is


$V_L = L \frac{di}{dt} = \frac{4}{10} \frac{d}{dt} [6(1 - e^{-5t})] = 12 e^{-5t}$

This question contains Statement-1 and Statement-2. Of the four choices given after the statements, choose the one that best describes the two statements.

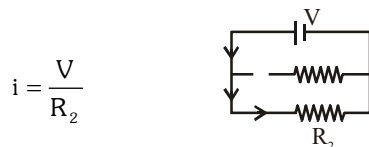
18. At  $t = 0$  inductor behaves as broken wire then



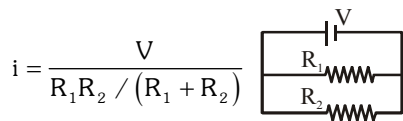at  $t = \infty$  Inductor behaves as conducting wire




19. Circuit can be reduced as

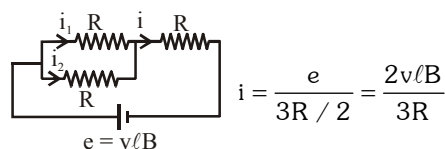

$i_1 = i_2 = \frac{i}{2} = \frac{v\ell B}{3R}$

20.  $e = B\ell v = (5 \times 10^{-5}) (2) (1.50) = 0.15 \text{ mV}$

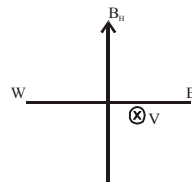
21.  $B = 0.3 \times 10^{-4} \text{ wb/m}^2$



$e = v\ell B = 5 \times 10^{-5} \times 0.3 \times 10^{-4} = 3 \text{ mV}$

22. Due to conducting nature of Al eddy currents are produced

23.

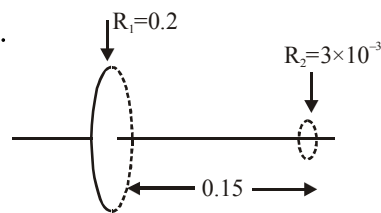


Mutual inductance =  $\frac{\mu_0 R_1^2 \pi R_2^2}{2(R_1^2 + X^2)^{3/2}}$

so flux through trigger coil =  $\left(\frac{\mu_0}{4\pi}\right) \cdot \frac{2\pi^2 R_1^2 R_2^2}{(R_1^2 + X^2)^{3/2}} i$

=  $\frac{10^{-7} \times (3.14)^2 (2 \times 10^{-1})^2 (3 \times 10^{-3})^2 \times 2 \times 2}{((0.2)^2 + (0.15)^2)^{3/2}}$

### ALTERNATING CURRENT

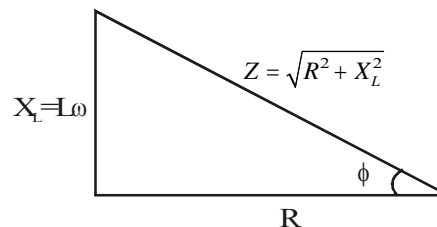24. On drawing the impedance triangle; we get



The power factor  $\cos \phi = \frac{R}{Z} = \frac{R}{\sqrt{R^2 + \omega^2 L^2}}$

26. Let  $Q_{\max} = Q_{\max}$

$\frac{1}{2} \frac{Q^2}{C} = \frac{1}{2} LI^2 \dots (i)$

[Given that energy stored in capacitor = Energy stored in conductor].

According to the conservation of energy we know

that  $\frac{1}{2} \frac{Q_{\max}^2}{C} = \frac{1}{2} \frac{Q^2}{C} + \frac{1}{2} LI^2$

$\frac{1}{2} \frac{Q_{\max}^2}{C} = \frac{1}{2} \frac{Q^2}{C} + \frac{1}{2} \frac{Q^2}{C}$  [from eq. (i)]

$\frac{Q_{\max}^2}{C} = \frac{2Q^2}{C}$

$Q^2 = \frac{Q_{\max}^2}{C}$

$Q = \frac{Q_{\max}}{\sqrt{2}}$

27. A DC meter measure the average value and the average value of AC over one full cycle is zero. Hence, DC meters can't measure AC.

28. Voltage across LC combination =  $|V_L - V_C|$   
 Voltage across LC combination =  $|50 - 50| = 0V$

29. The resonant frequency  $\omega_r = \frac{1}{\sqrt{LC}}$

$$\text{For } \omega_1 = \omega_2 \quad \frac{1}{\sqrt{L_1 C}} = \frac{1}{\sqrt{L_2 2C}}$$

On squaring both sides, we get

$$\frac{1}{L_1 C} = \frac{1}{L_2 (2C)}; \quad \frac{L_2}{L_1} = \frac{1}{2}; \quad L_2 = \frac{L_1}{2}$$

30. In order to transfer maximum power the generator should work at resonant frequency, i.e., C should be such so that

$$f = \frac{1}{2\pi\sqrt{LC}} \Rightarrow f^2 = \frac{1}{4\pi^2 LC}$$

$$\Rightarrow C = \frac{1}{4\pi^2 L f^2} = \frac{1}{4 \times 10 \times 10 \times 2500}$$

$$\Rightarrow C = 10^{-6} F = 1 \mu F$$

31. Power factor =  $\cos \phi = \frac{R}{Z}$

$$\cos \phi = \frac{12}{15} = \frac{4}{5} = 0.8$$

32. If resistance will be the part of circuit, phase difference between voltage and current can not be

$$\frac{\pi}{2}.$$

33. The voltage across L =  $V_L = IX_L$

$$\text{At resonance, current} = \frac{\text{Voltage}}{\text{Resistance}};$$

$$I = \frac{100V}{10^3 \Omega} = 0.1$$

$$\text{Also at resonance } X_L = X_C$$

$$X_C = \frac{1}{\omega C} = \frac{1}{200 \times 2 \times 10^{-6}} = \frac{10^4}{4} \Omega$$

$$V_L = IX_L = 0.1 \times \frac{10^4}{4} = 250V$$

34. Magnetic flux associated with rotating coil  
 =  $NBA \cos \omega t$   
 $\phi = NBA \cos \omega t$

$$\frac{d\phi}{dt} = -(NBA\omega) \sin(\omega t)$$

$$e = e_0 \sin \omega t$$

$$\text{Maximum value of emf generated in coil} \\ = NBA\omega$$

35. Given that  
 $E = E_0 \sin(\omega t)$  and  $I = I_0 \sin(\omega t - \pi/2)$

The phase difference between E and I is  $\frac{\pi}{2}$ .

Power dissipated in an AC circuit

$$P = E_{\text{rms}} I_{\text{rms}} \cos \phi = 0$$

So, power dissipated for this situation where phase

difference between voltage and current is  $\frac{\pi}{2}$  will be zero.

36.  $\tan \phi = \frac{X_L - X_C}{R}$

$$\tan 30 = \frac{X_C}{R} \Rightarrow X_C = \frac{R}{\sqrt{3}}$$

$$\tan 30 = \frac{X_L}{R} \Rightarrow X_L = \frac{R}{\sqrt{3}}$$

$$X_L = X_C \Rightarrow \text{Condition for resonance}$$

$$\text{So } \phi = 0$$

$$P = VI \cos 0$$

$$P = \frac{V^2}{R} = \frac{(220)^2}{200} = 242W$$


37. Energy is shared equally between L and C at

$$t = \frac{T}{8}, \frac{3T}{8}, \dots \text{ where } T = \frac{2\pi}{\omega} = 2\pi\sqrt{LC}$$

$$\text{so } t = \frac{T}{8} = \frac{2\pi\sqrt{LC}}{8} = \frac{\pi}{4}\sqrt{LC}$$

## EXERCISE -V-B

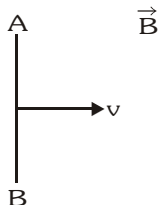1. A motional emf,  $e = B\ell v$  is induced in the rod. Or we can say a potential difference is induced between the two ends of the rod AB, with A at higher potential and B at lower potential. Due to this potential difference, there is an electric field in the rod.



2. Magnetic field produced by a current  $i$  in a large square loop at its centre.

$$B \propto \frac{i}{L} \text{ say } B = K \frac{i}{L}$$


$\therefore$  Magnetic flux linked with smaller loop,

$$\phi = B.S \Rightarrow \phi = \left( K \frac{i}{L} \right) (\ell^2)$$

Therefore, the mutual inductance

$$M = \frac{\phi}{i} = K \frac{\ell^2}{L} \Rightarrow M \propto \frac{\ell^2}{L}$$

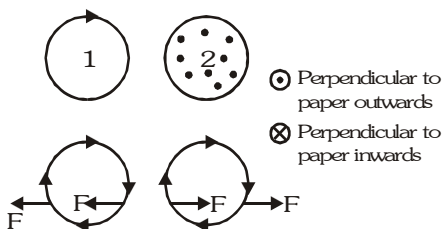3. For understanding, let us assume that the two loops are lying in the plane of paper as shown. The current in loop 1 will produce \* magnetic field in loop 2. Therefore, increase in current in loop 1 will produce an induced current in loop 2 which produce  $\otimes$  magnetic field passing through it i.e., induced current in loop 2 will also be clockwise as shown in the figure.



The loops will now repel each other as the currents at the nearest and farthest points of the two loops flow in the opposite directions.

4. The current-time ( $i$ - $t$ ) equation in L-R circuit is given by [Growth of current in L-R circuit]

$$i = i_0(1 - e^{-t/\tau_L}) \quad \dots(i)$$

where  $i_0 = \frac{V}{R} = \frac{12}{6} = 2A$

$$\text{and } \tau_L = \frac{L}{R} = \frac{8.4 \times 10^{-3}}{6} = 1.4 \times 10^{-3}s$$

$$\text{and } i = 1A \quad (\text{given})$$

Substituting these values in equation (i), we get

$$t = 0.97 \times 10^{-3}s$$

$$\Rightarrow t = 0.97 \text{ ms} \Rightarrow t \approx 1\text{ms}$$

$$5. \quad \int \vec{E} \cdot d\vec{\ell} = \left| \frac{d\phi}{dt} \right| = S \left| \frac{dB}{dt} \right|$$

$$\Rightarrow E(2\pi r) = \pi a^2 \left| \frac{dB}{dt} \right| \text{ for } r \geq a \therefore E = \frac{a^2}{2r} \left| \frac{dB}{dt} \right|$$

$$\therefore \text{Induced electric field} \propto \frac{1}{r}$$


$$\text{For } r \leq a; E(2\pi r) = \pi r^2 \left| \frac{dB}{dt} \right| \Rightarrow E = \frac{r}{2} \left| \frac{dB}{dt} \right| \Rightarrow E \propto r$$

$$\text{At } r = a, E = \frac{a}{2} \left| \frac{dB}{dt} \right|$$

Therefore, variation of

$E$  with  $r$ (distance from

centre) will be as follows :

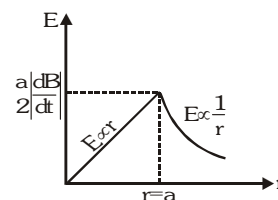

6. The equations of  $I_1(t)$ ,  $I_2(t)$  and  $B(t)$  will take the following forms :

$$I_1(t) = K_1(1 - e^{-k_2 t}) \rightarrow \text{current growth in L-R circuit}$$

$$B(t) = K_3(1 - e^{-k_2 t}) \rightarrow B(t) \rightarrow I_1(t); B = \mu_0 Ni \text{ in case of}$$

$$\text{solenoid coil and } \frac{\mu_0 Ni}{2R} \text{ in case of circular coil i.e.,}$$


$$B \propto i \Rightarrow I_2(t) = K_4 e^{-k_2 t}$$

$$\left[ I_2(t) = \frac{e_2}{R} \text{ and } e_2 \propto \frac{dI_1}{dt} : e_2 = -M \frac{dI_1}{dt} \right]$$

$$\text{Therefore the product } I_2(t) B(t) = K_5 e^{-k_2 t} (1 - e^{-k_2 t}).$$

The value of this product is zero at  $t=0$  and  $t=\infty$ . Therefore, the product will pass through a maximum value ( $K_1 : K_2 : K_3 : K_4$  and  $K_5$  are positive constants and  $M$  is the mutual inductance between the coil and the ring).

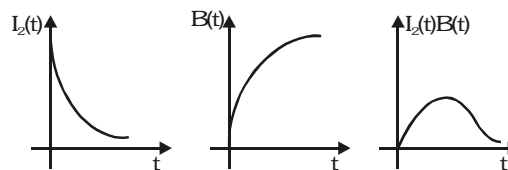The corresponding graph will be as follows :



7. Electric field will be induced in both AD and BC.
8. When current flows in any of the coils, the flux linked with the other coil will be maximum in the first case. Therefore, mutual inductance will be maximum in case (a).
9. When switch S is closed magnetic field lines passing through Q increases in the direction from right to left. So, according to Lenz's law induced current in Q i.e.,  $I_{Q_2}$  will flow in such a direction, so that the magnetic field lines due to  $I_{Q_2}$  passes from left to right through Q. This is possible when  $I_{Q_1}$  flows in anticlockwise direction as seen by E. Opposite is the case when switch S is opened i.e.,  $I_{Q_2}$  will be clockwise as seen by E.

10. Power  $P = \frac{e^2}{R}$

Here,  $e = \text{induced emf} = \left( \frac{d\phi}{dt} \right)$

where  $\phi = NBA$   $e = -NA \left( \frac{dB}{dt} \right)$

Also,  $R \propto \frac{1}{r^2}$

where  $R = \text{resistance}$ ,  $r = \text{radius}$ ,  $\ell = \text{length}$

$\therefore P \propto \frac{N^2 r^2}{\ell} \therefore \frac{P_1}{P_2} = 1$

11. As the current  $i$  leads the emf  $e$  by

$\frac{\pi}{4}$ , it is an R-C circuit.  $\tan \phi = \frac{X_C}{R}$

or  $\tan \frac{\pi}{4} = \frac{1}{\omega C R} \therefore \omega C R = 1$

As  $\omega = 100 \text{ rad/s}$

The product of C-R should be  $\frac{1}{100} \text{ s}^{-1}$ .

12. Polarity of emf will be opposite in the two case while entering and while leaving the coil. Only in option (b) polarity is changing.
13. In uniform magnetic field, change in magnetic flux is zero. Therefore, induced current will be zero.
14. As area of outer loop is bigger therefore emf induced in outer loop is dominant and therefore according to lenz law current in outer loop is Anticlockwise and inner loop is clockwise

### MCQ

1. Electrostatic and gravitational field do not make closed loops.

3. When resistivity is low current induced will be more; therefore impulsive force on the ring will also be more and it jumps to higher levels. [But for this mass should be either less or equal to the other]

### Comprehension#1

1. Charge on capacitor at time  $t$  is :

$$q = q_0(1 - e^{-t/\tau})$$

Here,  $q_0 = CV$  and  $t = 2\tau$

$$\therefore q = CV(1 - e^{-2\tau/\tau}) = CV(1 - e^{-2})$$

2. From conservation of energy,


$$\frac{1}{2} L I_{\max}^2 = \frac{1}{2} C V^2 \therefore I_{\max} = V \sqrt{\frac{C}{L}}$$

3. Comparing the LC oscillations with normal SHM we get,

$$\frac{d^2 Q}{dt^2} = -\omega^2 Q \text{ Here, } \omega^2 = \frac{1}{LC} \therefore Q = -LC \frac{d^2 Q}{dt^2}$$

### Subjective

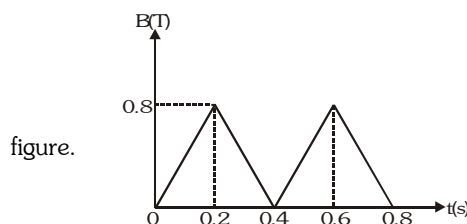1. Magnetic field (B) varies with time (t) as shown in



$$\left| \frac{dB}{dt} \right| = \frac{0.8}{0.2} = 4 \text{ T/s}$$

Induced emf in the coil due to change in magnetic flux passing through it,

$$e = \left| \frac{d\phi}{dt} \right| = NA \left| \frac{dB}{dt} \right|$$

Here,  $A = \text{Area of coil} = 5 \times 10^{-3} \text{ m}^2$

$N = \text{Number of turns} = 100$

Substituting the values, we get

$$e = (100)(5 \times 10^{-3})(4) \text{ V} = 2 \text{ V}$$

Therefore, current passing through the coil


$$i = \frac{e}{R} \text{ (R = Resistance of coil} = 1.6 \Omega)$$

$$\Rightarrow i = \frac{2}{1.6} = 1.25 \text{ A}$$

Note that from 0 to 0.2 s and from 0.4 s to 0.6 s, magnetic field passing through the coil increases, while during the time 0.2 s to 0.4 s and from 0.6 s to 0.8 s magnetic field passing through the coil decreases. Therefore, direction of current through



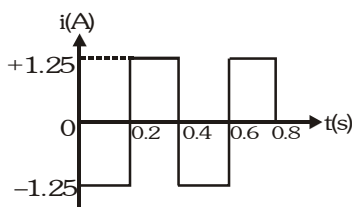the coil in these two time intervals will be opposite to each other. the variation of current ( $i$ ) with time ( $t$ ) will be as follows :



Power dissipated in the coil is

$$P = i^2 R = (1.25)^2 (1.6) \text{ W} = 2.5 \text{ W}$$

Power is independent of the direction of current through the coil. Therefore, power ( $P$ ) versus time ( $t$ ) graph for first two cycles will be as follows :



Total heat obtained in 12,000 cycles will be

$$H = P \cdot t = (2.5) (12000) (0.4) = 12000 \text{ J}$$

This heat is used in raising the temperature of the coil and the water. Let  $\theta$  be the final temperature. Then  $H = m_w S_w (\theta - 30) + m_c S_c (\theta - 30)$

Here  $m_w$  = mass of water = 0.5 kg

$S_w$  = specific heat of water = 4200 J/kg-K

$m_c$  = mass of coil = 0.06 kg

and  $S_c$  = specific heat of coil = 500 J/kg-K


Substituting the values, we get

$$1200 = (0.5) (4200) (\theta - 30) + (0.06) (500) (\theta - 30)$$

$$\Rightarrow \theta = 35.6^\circ \text{C}$$

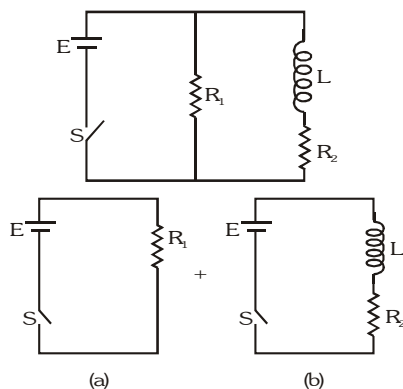2. (a) Given  $R_1 = R_2 = 2\Omega$ ,  $E = 12\text{V}$

and  $L = 400 \text{ mH} = 0.4 \text{ H}$ . Two parts of the circuit are in parallel with the applied battery. So, the upper circuit can be broken as :



Now refer figure (b) :

This is a simple L-R circuit, whose time constant

$$\tau_L = L / R_2 = \frac{0.4}{2} = 0.2 \text{ s}$$

and steady state current  $i_0 = E / R_2 = 12 / 2 = 6 \text{ A}$

Therefore, if switch S is closed at time  $t=0$ , then current in the circuit at any time  $t$  will be given by

$$i(t) = i_0 (1 - e^{-t/\tau_L})$$

$$i(t) = 6 (1 - e^{-t/0.2}) = 6(1 - e^{-5t}) = i \quad (\text{say})$$


Therefore, potential drop across L at any time  $t$  is:

$$V = L \left| \frac{di}{dt} \right| = L(30e^{-5t}) = (0.4)(30)e^{-5t}$$

$$\Rightarrow V = 12e^{-5t} \text{ volt}$$

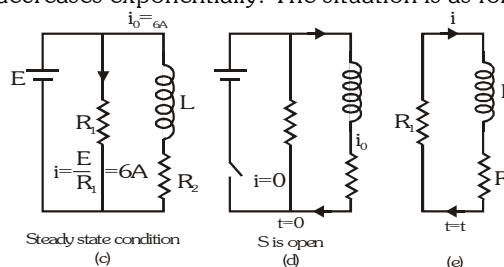(b) The steady state current in L or  $R_2$  is  $i = 6 \text{ A}$

Now, as soon as the switch is opened, current in  $R_1$  is reduced to zero immediately. But in L and  $R_2$  it decreases exponentially. The situation is as follows:



Refer figure (e) :

Time constant of this circuit would be

$$\tau_L' = \frac{L}{R_1 + R_2} = \frac{0.4}{(2 + 2)} = 0.1 \text{ s}$$

$\therefore$  Current through  $R_1$  at any time  $t$  is

$$i = i_0 e^{-t/\tau_L'} = 6e^{-t/0.1} \Rightarrow i = 6e^{-10t} \text{ A}$$

Direction of current in  $R_1$  is as shown in figure or clockwise.

3. (i) Applying Kirchhoff's second law :

$$\frac{d\phi}{dt} - iR - L \frac{di}{dt} = 0 \Rightarrow \frac{d\phi}{dt} = iR + L \frac{di}{dt} \quad \dots(i)$$

This is the desired relation between  $i$ ,  $\frac{di}{dt}$  and  $\frac{d\phi}{dt}$ .

(ii) equation (1) can be written as

$$d\phi = iRdt + Ldi$$

Integrating we get,  $\Delta\phi = R \cdot \Delta q + Li$

$$\Delta q = \frac{\Delta\phi}{R} - \frac{Li_1}{R} \quad \dots(ii)$$

$$\text{Here, } \Delta\phi = \phi_f - \phi_i = \int_{x=2x_0}^{x=x_0} \frac{\mu_0 I_0}{2\pi x} \ell dx = \frac{\mu_0 I_0 \ell}{2\pi} \ln(2)$$

So, from Equation (ii) charge flown through the resistance upto time  $t=T$ , when current is  $i_1$ , is-

$$\Delta q = \frac{1}{R} \left[ \frac{\mu_0 I_0 \ell}{2\pi} \ln(2) - Li_1 \right]$$

(iii) This is the case of current decay in an L-R circuit.

$$\text{Thus, } i = i_0 e^{-t/\tau_L} \quad \dots \text{(iii)}$$

$$\text{Here, } i = \frac{i_1}{4}, i_0 = i_1, t = (2T - T) = T \text{ and } \tau_L = \frac{L}{R}$$

Substituting these values in equation (3), we get :

$$\tau_L = \frac{L}{R} = \frac{T}{\ln 4}$$

4. (i) For a element strip of thickness  $dx$  at a distance  $x$  from left wire, net magnetic field (due to both wires)

$$B = \frac{\mu_0 I}{2\pi x} + \frac{\mu_0 I}{2\pi (3a - x)}$$

(outwards)

$$= \frac{\mu_0 I}{2\pi} \left( \frac{1}{x} + \frac{1}{3a - x} \right)$$

Magnetic flux in this strip,

$$d\phi = BdS = \frac{\mu_0 I}{2\pi} \left( \frac{1}{x} + \frac{1}{3a - x} \right) a dx$$

$$\therefore \text{ total flux } \phi = \int_a^{2a} d\phi = \frac{\mu_0 Ia}{2\pi} \int_a^{2a} \left( \frac{1}{x} + \frac{1}{3a - x} \right) dx$$

$$\phi = \frac{\mu_0 Ia}{\pi} \ln(2) \quad \phi = \frac{\mu_0 a \ell n(2)}{\pi} (I_0 \sin \omega t) \quad \dots \text{(i)}$$

Magnitude of induced emf,

$$e = \left| -\frac{d\phi}{dt} \right| = \frac{\mu_0 a I_0 \omega \ell n(2)}{\pi} \cos \omega t = e_0 \cos \omega t$$

$$\text{where } e_0 = \frac{\mu_0 a I_0 \omega \ell n(2)}{\pi}$$

Charge stored in the capacitor,

$$q = Ce = C e_0 \cos \omega t \quad \dots \text{(ii)}$$

$$\text{and current in the loop } i = \frac{dq}{dt} = C \omega e_0 \sin \omega t \quad \dots \text{(iii)}$$

$$i_{\max} = C \omega e_0 = \frac{\mu_0 a I_0 \omega^2 C \ell n(2)}{\pi}$$

(ii) Magnetic flux passing through the square loop


$$\phi \propto \sin \omega t \quad [\text{From equation (i)}]$$

i.e., \* magnetic field passing through the loop is increasing at  $t=0$ . Hence, the induced current will produce  $\otimes$  magnetic field (from Lenz's law). Or the current in the circuit at  $t=0$  will be clockwise (or negative as per the given convention). Therefore, charge on upper plate could be written as,

$$q = +q_0 \cos \omega t \quad [\text{From equation (ii)}]$$

$$\text{Here, } q_0 = C e_0 = \frac{\mu_0 a C I_0 \omega \ell n(2)}{\pi}$$

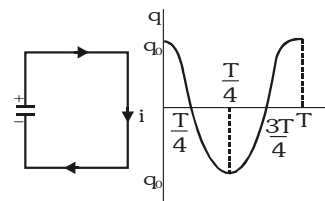The corresponding  $q$ - $t$  graph is shown in figures.



5. After a long time, resistance across an inductor becomes zero while resistance across capacitor becomes infinite. Hence, net external resistance,

$$R_{\text{net}} = \frac{R}{2} + R = \frac{3R}{4} \quad \text{Current through the batteries,}$$

$$i = \frac{2E}{\frac{3R}{4} + r_1 + r_2} \quad \text{Given that potential across the terminals of cell A is zero.}$$

$$\therefore E - ir_1 = 0 \Rightarrow E - \left( \frac{2E}{3R/4 + r_1 + r_2} \right) r_1 = 0$$

$$\text{Solving this equation, we get } R = \frac{4}{3} (r_1 - r_2)$$

6. Inductive reactance

$$X_L = \omega L = (50) (2\pi) (35 \times 10^{-3}) \approx 11 \Omega$$

Impedance

$$Z = \sqrt{R^2 + X_L^2} = \sqrt{(11)^2 + (11)^2} = 11\sqrt{2} \Omega$$

Given  $v_{\text{rms}} = 220\text{V}$  Hence, amplitude of voltage

$$v_0 = \sqrt{2} v_{\text{rms}} = 220\sqrt{2}\text{V}$$


$$\therefore \text{ Amplitude of current } i_0 = \frac{v_0}{Z} = \frac{220\sqrt{2}}{11\sqrt{2}} = 20\text{A}$$

$$\text{Phase difference } \phi = \tan^{-1} \left( \frac{X_L}{R} \right) = \tan^{-1} \left( \frac{11}{11} \right) = \frac{\pi}{4}$$

In L-R circuit voltage leads the current. Hence, instantaneous current in the circuit is,

$$i = (20\text{A}) \sin (\omega t - \pi/4)$$

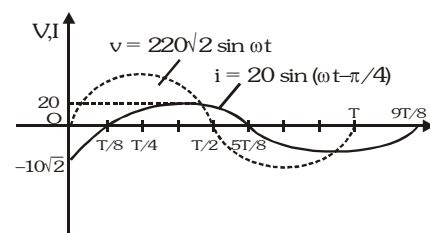Corresponding  $i$ - $t$  graph is shown in figure.



7. Out side the solenoid net magnetic field zero. It can be assumed only inside the solenoid and equal to  $\mu_0 nI$ .

$$\text{induced } e = -\frac{d}{dt} = -\frac{d}{dt}(BA) = -\frac{d\phi}{dt}(\mu_0 n / \pi a^2)$$

$$\text{or } |e| = (\mu_0 n \pi a^2) (I_0 \omega \cos \omega t)$$

$$\text{Resistance of the cylindrical vessel } R = \frac{\rho \ell}{s} = \frac{\rho(2\pi R)}{Ld}$$

$$\therefore \text{ Induced current } i = \frac{|e|}{R} = \frac{\mu_0 L d n a^2 I_0 \omega \cos \omega t}{2\rho R}$$

8. This is a problem of L-C oscillations.

Charge stored in the capacitor oscillates simple harmonically as  $Q = Q_0 \sin(\omega t + \phi)$

Here,  $Q_0 = \text{max. value of } Q = 200 \mu\text{C} = 2 \times 10^{-4} \text{ C}$

$$\omega = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(2 \times 10^{-3} \text{ H})(5.0 \times 10^{-6} \text{ F})}} = 10^4 \text{ s}^{-1}$$

Let at  $t=0$ ,  $Q=Q_0$  then

$$Q(t) = Q_0 \cos \omega t \dots (i) \quad I(t) = \frac{dQ}{dt} = -Q_0 \omega \sin \omega t \dots (ii)$$

$$\text{and } \frac{dI(t)}{dt} = -Q_0 \omega^2 \cos(\omega t) \dots (iii)$$

$$(i) \quad Q = 100 \mu\text{C} \Rightarrow \frac{Q_0}{2} \quad \text{At } \cos \omega t = \frac{1}{2} \Rightarrow \omega t = \frac{\pi}{3}$$

At  $\cos(\omega t) = \frac{1}{2}$ , from equation (iii) :

$$\left| \frac{dI}{dt} \right| = (2.0 \times 10^{-4} \text{ C})(10^4 \text{ s}^{-1})^2 \left( \frac{1}{2} \right) = 10^4 \text{ A/s}$$

(ii)  $Q=200\mu\text{C}$  or  $Q_0$  when  $\cos(\omega t)=1$  i.e.  $\omega t=0, 2\pi, \dots$

At this time  $I(t) = -Q_0 \omega \sin \omega t \Rightarrow I(t) = 0$

$[\sin 0 = \sin 2\pi = 0]$

(iii)  $I(t) = -Q_0 \omega \sin \omega t$

$\therefore$  Maximum value of  $I$  is  $Q_0 \omega$

$$I_{\text{max}} = Q_0 \omega = (2.0 \times 10^{-4} \text{ C})(10^4 \text{ s}^{-1}) \Rightarrow I_{\text{max}} = 2.0 \text{ A}$$

(iv) From energy conservation

$$\frac{1}{2} L I_{\text{max}}^2 = \frac{1}{2} L I^2 + \frac{1}{2} \frac{Q^2}{C}$$


$$\Rightarrow Q = \sqrt{LC(I_{\text{max}}^2 - I^2)} \quad \left[ I = \frac{I_{\text{max}}}{2} = 1.0 \text{ A} \right]$$

$$\therefore Q = \sqrt{(2.0 \times 10^{-3})(5.0 \times 10^{-6})(2^2 - 1^2)}$$

$$Q = \sqrt{3} \times 10^{-4} \text{ C} = 1.732 \times 10^{-4} \text{ C}$$

$$11. \quad \text{induce electric field} = \frac{R}{2} \frac{dB}{dt} = \frac{BR}{2}$$
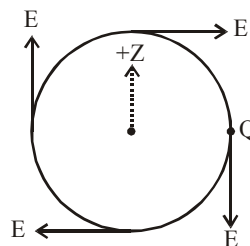
$$\text{torque on charge} = \frac{QBR^2}{2}(-\vec{k})$$



$$\text{by } \vec{\tau} = \frac{d\vec{L}}{dt} \Rightarrow \int d\vec{L} = \int_0^1 \vec{\tau} dt$$


$$\Delta \vec{L} = \frac{QBR^2}{2}(-\vec{k})$$

Change magnetic dipole moment =  $\gamma \Delta \vec{L}$

$$\frac{\gamma QBR^2}{2}(-\vec{k})$$

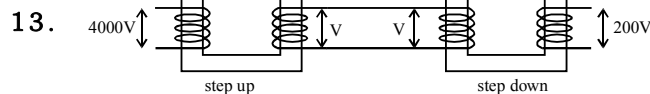12. Magnitude of induced electric field =

$$\frac{R}{2} \frac{dB}{dt} = \frac{BR}{2}$$



13.

for step up transformer

$$\frac{V}{4000} = \frac{10}{1} \Rightarrow V = 40,000 \text{ Volt}$$

for step down transformer

$$\frac{N_1}{N_2} = \frac{V}{200} = \frac{4000}{200} = 200$$

14. Current in transmission line

$$= \frac{\text{Power}}{\text{Voltage}} = \frac{600 \times 10^3}{40,000} = 150 \text{ A}$$

Resistance of line =  $0.4 \times 20 = 8 \Omega$

Power loss in line =  $i^2 R = (150)^2 \times 8 = 180 \text{ KW}$

percentage of power dissipation in during

$$\text{transmission} = \frac{180 \times 10^3}{600 \times 10^3} \times 100 = 30\%$$