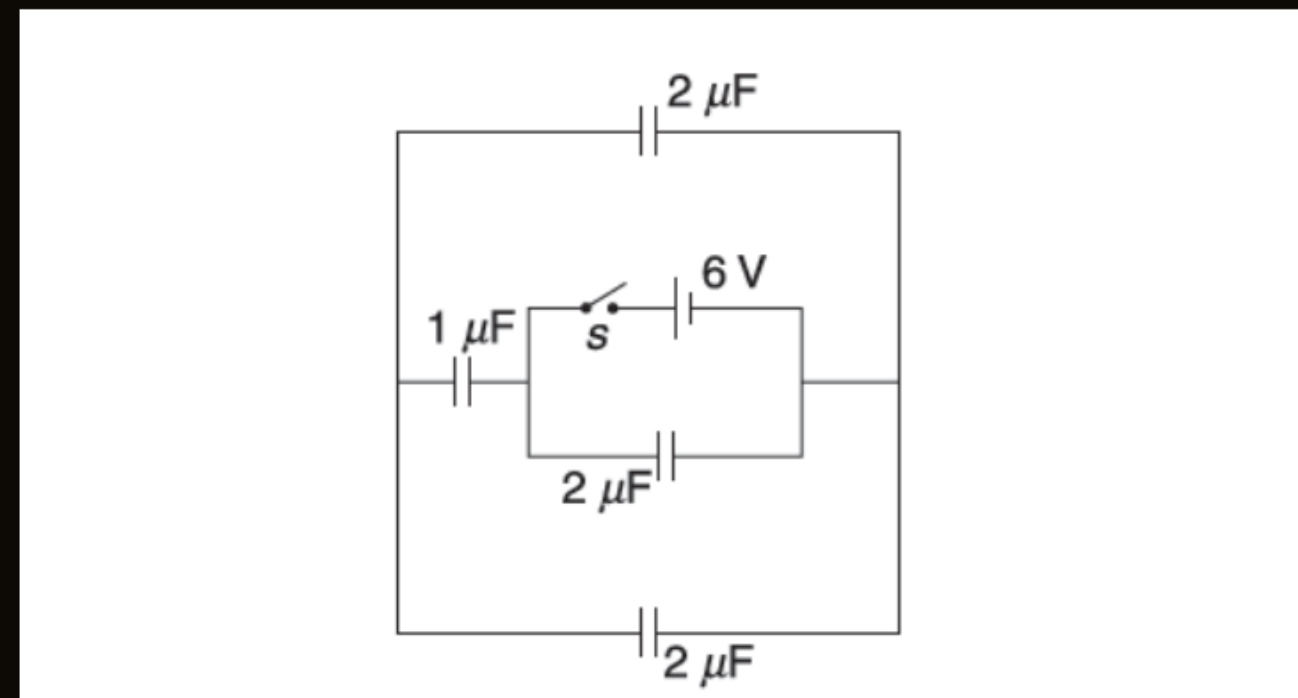



$$C_{eq} = \frac{4 \times 1}{4 + 1} = \frac{4}{5} \mu\text{F}$$

$$Q = C_{eq} V = \frac{4}{5} \mu\text{F} \times 6\text{V} \\ = \frac{24}{5} \mu\text{C} = \underline{4.8 \mu\text{C}}$$

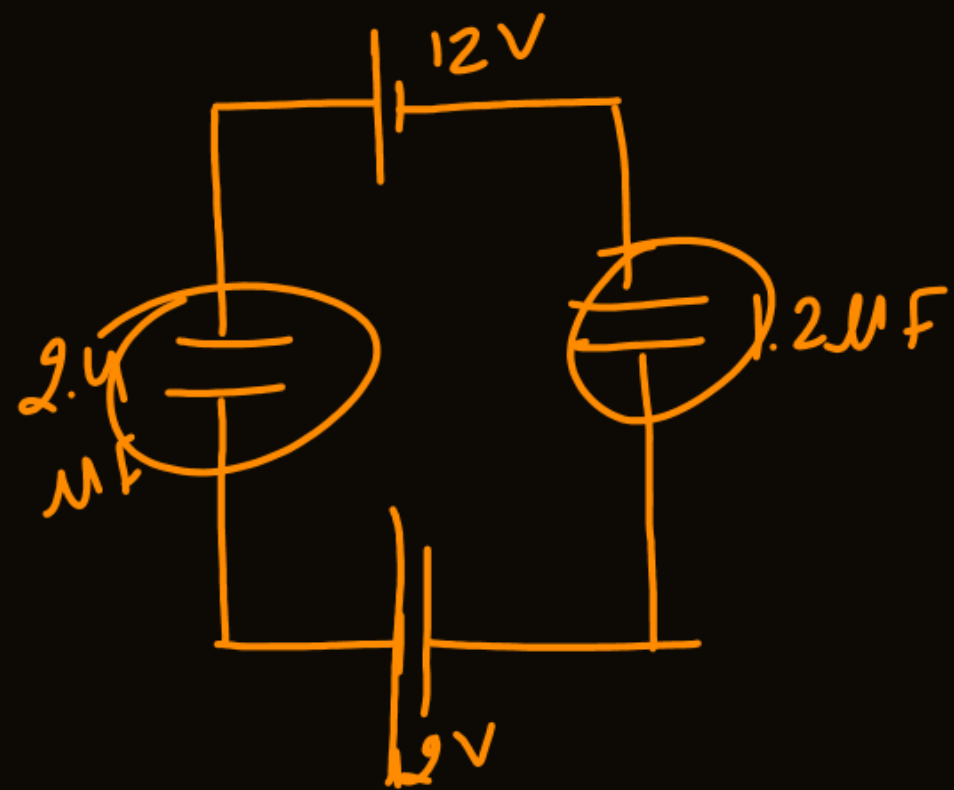Q. 13: Find charge supplied by the cell after the switch is closed.



$$Q_{net} = 12 + 4.8 \\ = \underline{16.8 \mu\text{C}}$$




$$\mathcal{E}_g = 0$$

$$\mathcal{Q} = 0$$

$$\frac{4 \times 2}{6 \times 3} = \frac{4}{3} \mu F$$

$$Q_1 = 12V \times \frac{4}{3} \mu F$$

$$= 16 \mu C$$

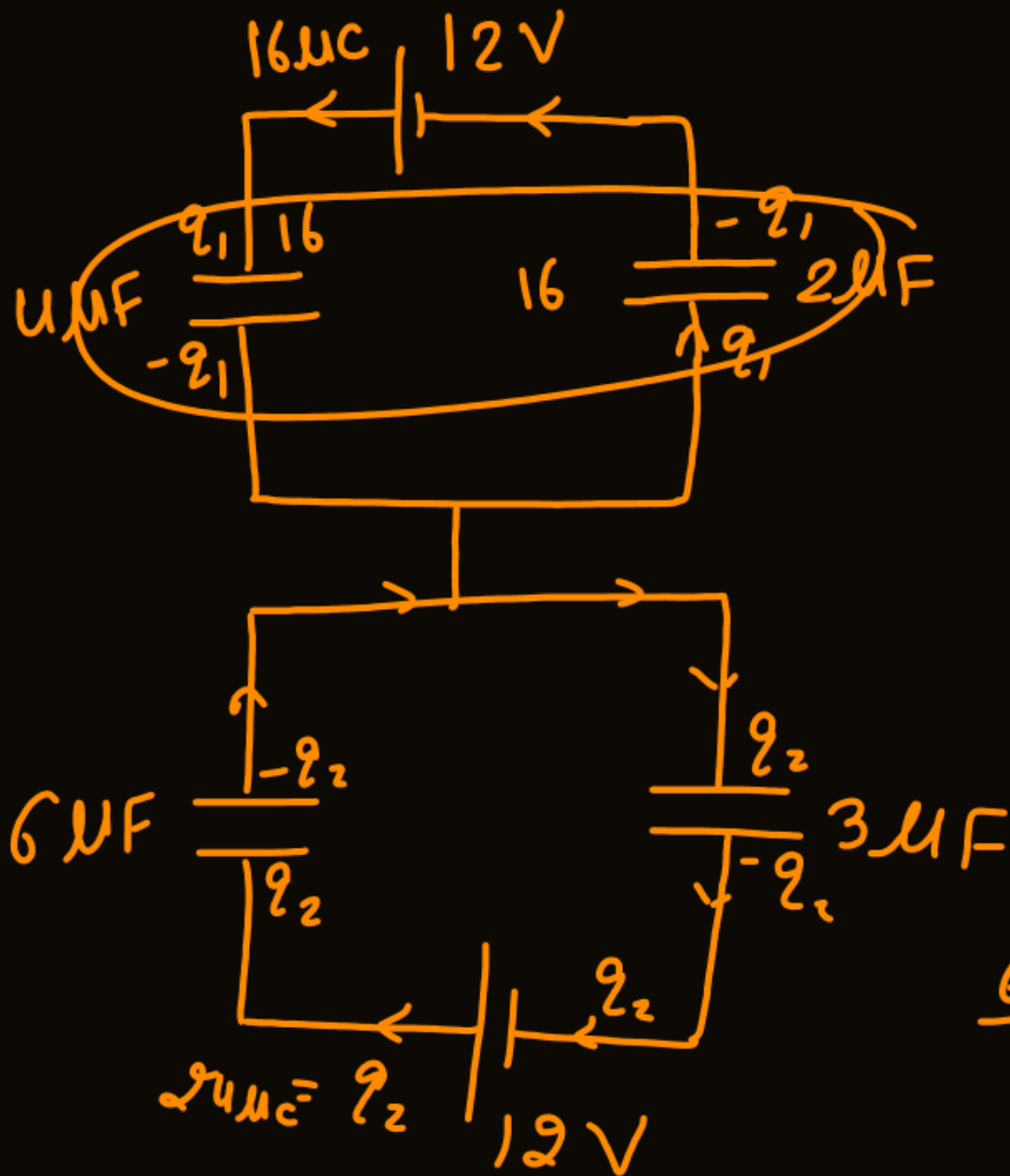

$$W_B = \Delta U + \text{Heat}$$

$$12 \times 16 \mu J + 12 \times 24 \mu J =$$

$$\text{Heat} = 240 \mu J$$


$$\frac{6 \times 3}{9} = 2 \mu F$$


$$Q_2 = 2 \times 12 = 24 \mu C$$

$$\frac{(16)^2}{2 \times 4/3} \mu J + \frac{(24)^2}{2 \times 2} + \text{Heat}$$

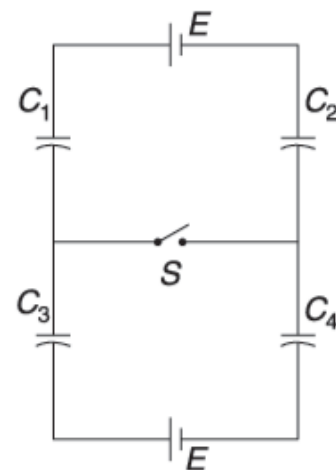Q. 18: In the circuit shown in Figure $E = 12 \text{ V}$, $C_1 = 4 \mu F$, $C_2 = 2 \mu F$, $C_3 = 6 \mu F$ and $C_4 = 3 \mu F$.

Find the heat produced in the circuit after switch S is shorted.



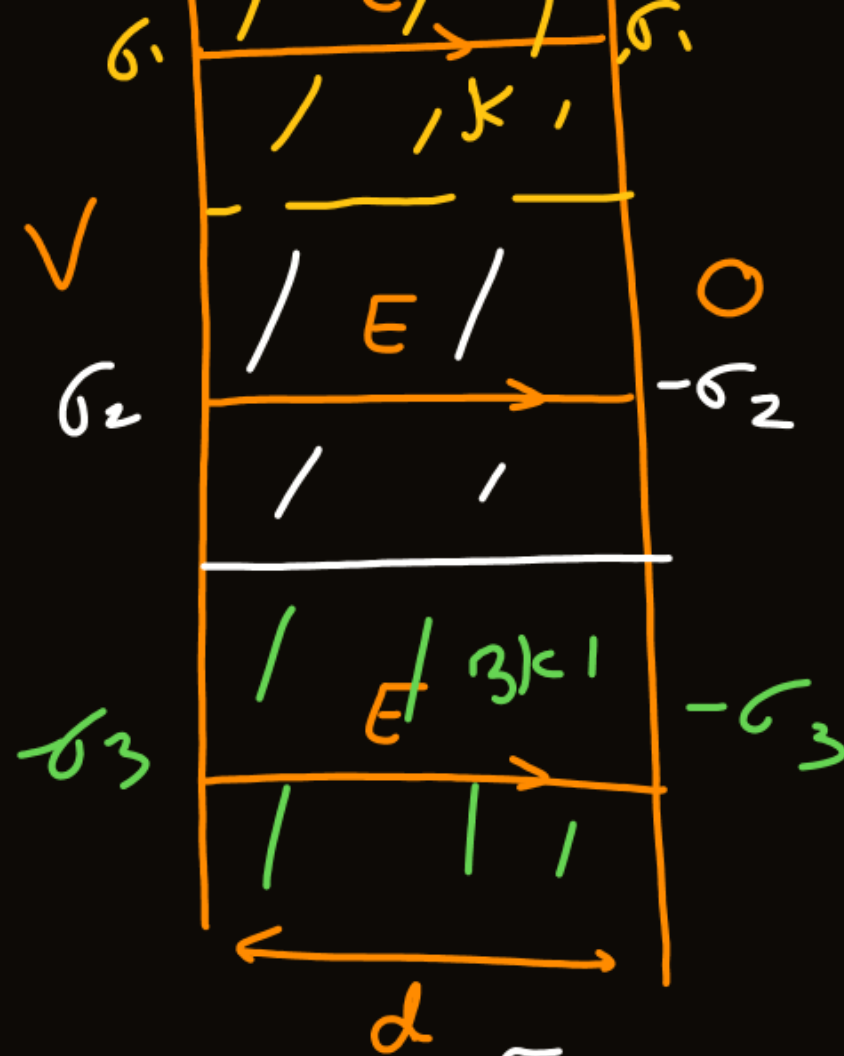


$$\frac{E_0}{2k} = \frac{V}{d}$$

$$E_0 = \frac{2kV}{d}$$

$$d \quad \epsilon_0 k \quad \epsilon_0 2k \quad \epsilon_0 3k$$
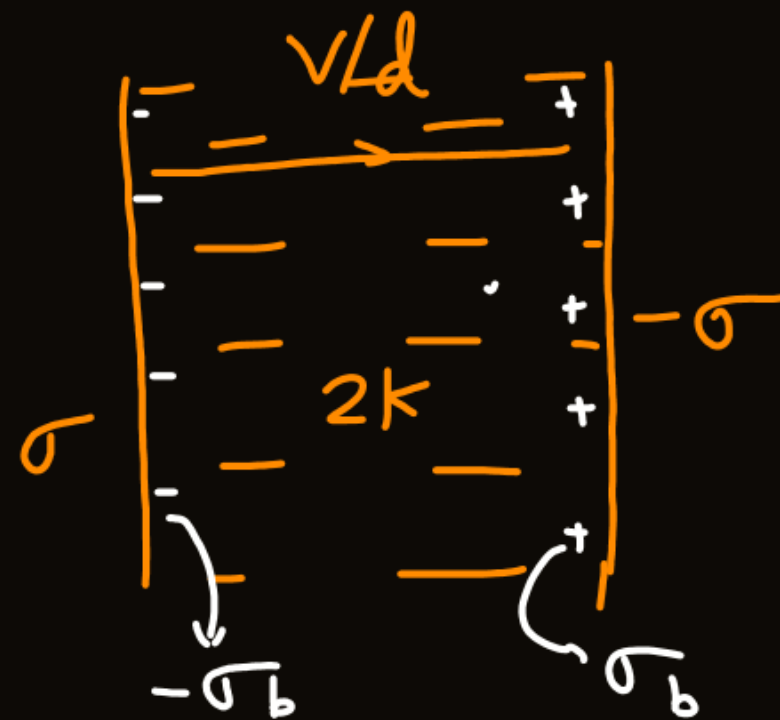
$$\sigma_1 : \sigma_2 : \sigma_3 = 1 : 2 : 3$$



$$\frac{\sigma}{\epsilon_0} = E_0 \quad (\rightarrow)$$


$$\frac{\sigma_b}{\epsilon_0} = E' \quad (\leftarrow)$$

$$E = E_0 - E' = \frac{E_0}{(2k)} = \frac{V}{d} \Rightarrow \frac{2kV}{d} - E' = \frac{V}{d}$$

$$E' = (2k-1) \frac{V}{d} = \frac{\sigma_b}{\epsilon_0}$$

$$\sigma_b = (2k-1) \frac{V}{d} \epsilon_0$$

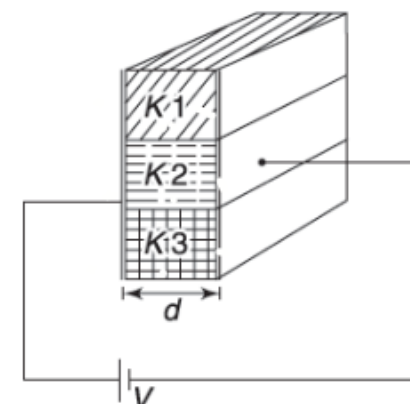- density on the surface of the capacitor plate.
- (b) Calculate the surface charge density of bound (induced) charge on the middle dielectric.
- (c) If the three dielectrics occupy equal volume between the plates, calculate the capacitance of the capacitor.



$$C_{eq} = C_1 + C_2 + C_3$$
$$= \frac{k \frac{A}{3} \epsilon_0}{d} + \frac{2k \frac{A}{3} \epsilon_0}{d} + \frac{3k \frac{A}{3} \epsilon_0}{d}$$

$$= \frac{k A \epsilon_0}{3d} \{1+2+3\}$$

$$= \frac{2k A \epsilon_0}{d}$$

Q. 22: A parallel plate capacitor has square plates of side length L . Plates are kept vertical at separation d between them. The space between the plates is filled with a dielectric whose dielectric constant (K) changes with height (x) from

the lower edge of the plates as $K = e^{\beta x}$ where β is a positive constant. A potential difference of V is applied across the capacitor plates.

- Plot the variation of surface charge density (σ) on the positive plate of the capacitor versus x .
- Plot the variation of electric field between the plates as a function of x .
- Calculate the capacitance of the capacitor.

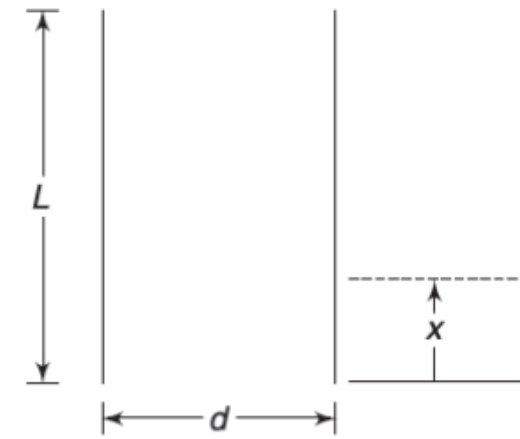


Diagram of the capacitor showing two vertical plates of length L and separation d . A potential difference V is applied across the plates. A small element of height dx is shown at height x from the bottom edge. The electric field E is indicated as $E = \frac{V}{d}$.

$$dC = \frac{\epsilon^{\beta x} L dx \epsilon_0}{d}$$


$$dq = (dC) V$$

$$= \frac{\epsilon^{\beta x} L dx \epsilon_0 V}{d}$$

$$\sigma = \frac{dq}{dA} = \frac{\epsilon^{\beta x} L dx \epsilon_0 V}{d L dx}$$

$$\sigma = \frac{\epsilon_0 V}{d} e^{\beta x}$$

Diagram showing the variation of electric field E versus height x . The electric field is constant and equal to $\frac{V}{d}$ for all values of x from 0 to L .

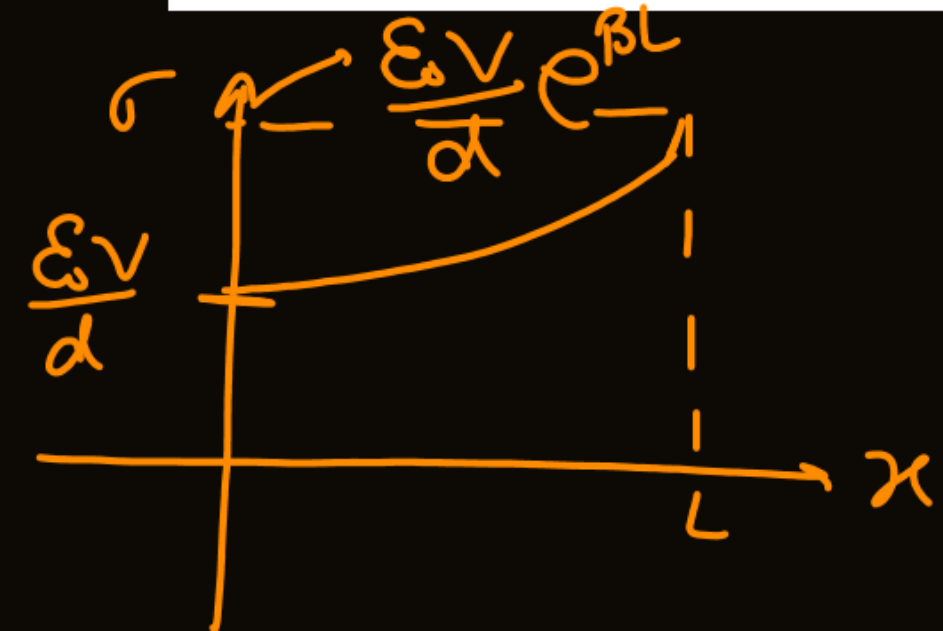



$$C = \int dc = \frac{L \epsilon_0}{d} \int_0^L e^{\beta x} dx$$

$$= \frac{L \epsilon_0}{d} \left(\frac{e^{\beta x}}{\beta} \right)_0^L$$

$$C = \frac{L \epsilon_0}{\beta d} \{ e^{\beta L} - 1 \}$$

Q. 42: Four large identical metallic plates are placed as shown in the Figure. Plate 2 is given a charge Q . All other plates are neutral. Now plates 1 and 4 are earthed. Area of each plate is A .

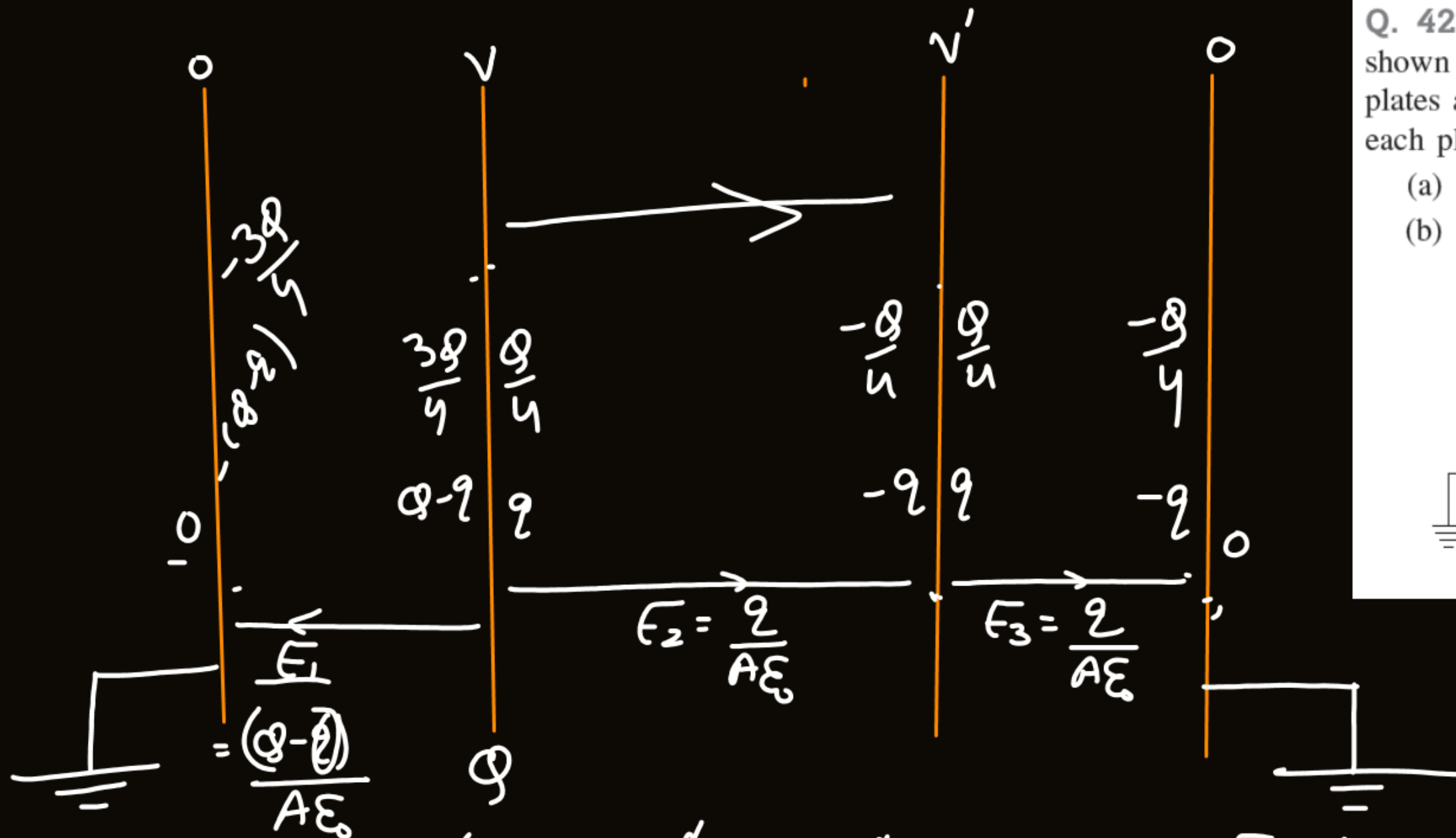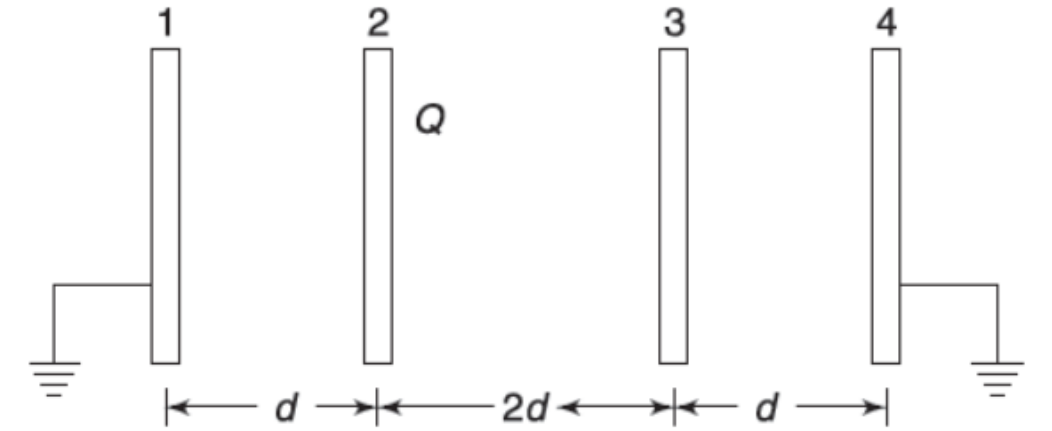- (a) Find charge appearing on right side of plate 3.
 (b) Find potential difference between plates 1 and 2.




$$E_1 d = E_2 2d + E_3 d$$

$$Q - q = 2q + q$$

$$q = Q/4$$

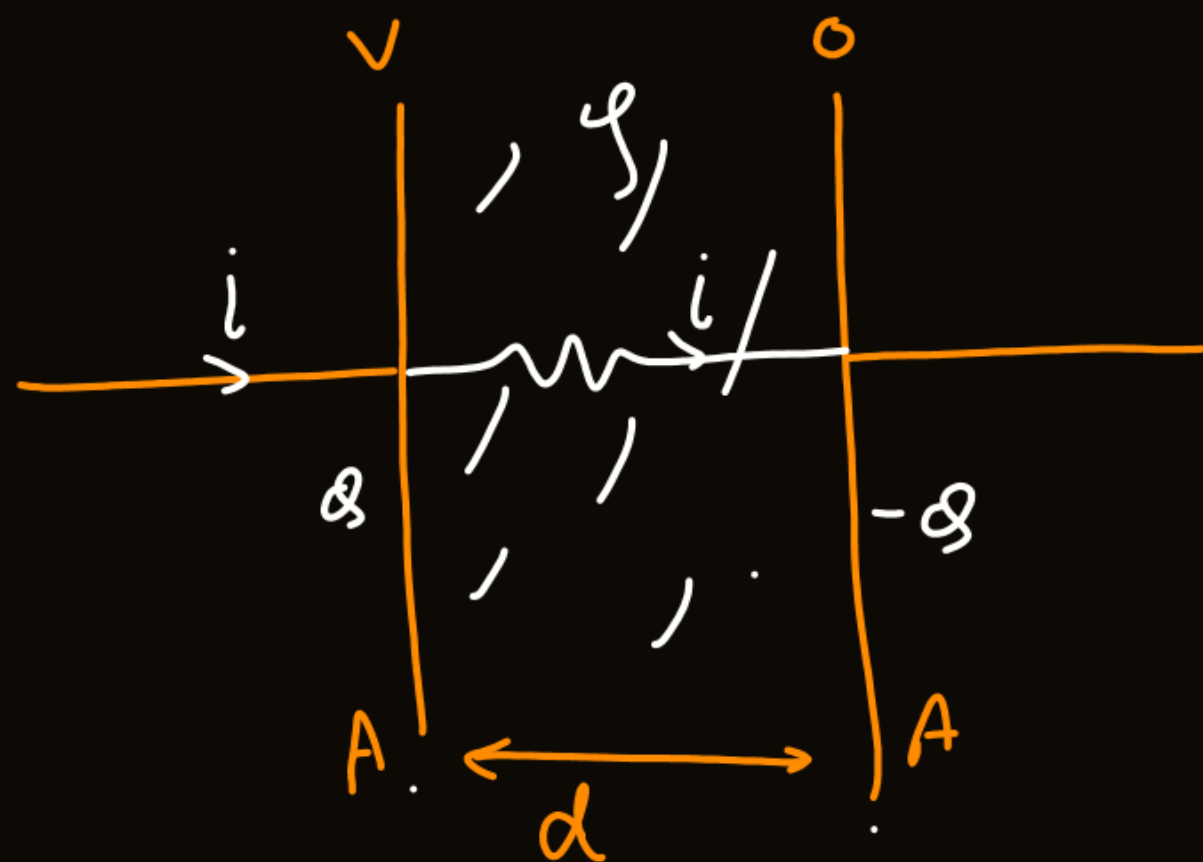
$$V = E_1 d = \frac{3Q}{4A\epsilon_0} d$$



$$i = \frac{VA}{\rho d}$$

$$Q = CV = \frac{KA\epsilon_0}{d} V$$

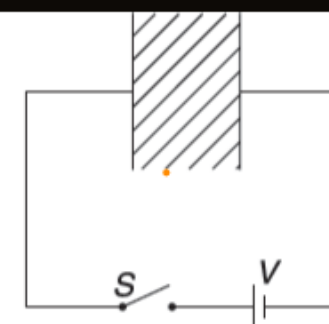
Q. 44: A parallel plate capacitor has plate area A and separation between the plates equal to d . A material of dielectric constant K and resistivity ρ is filled between the plates. The switch is closed to connect the capacitor to a cell of emf V .



- Write the steady state current in the circuit and charge on the capacitor.
- When the circuit is in steady state, switch s is opened (at $t = 0$). Write charge on the capacitor as function of time (t) after this.



$t=0$

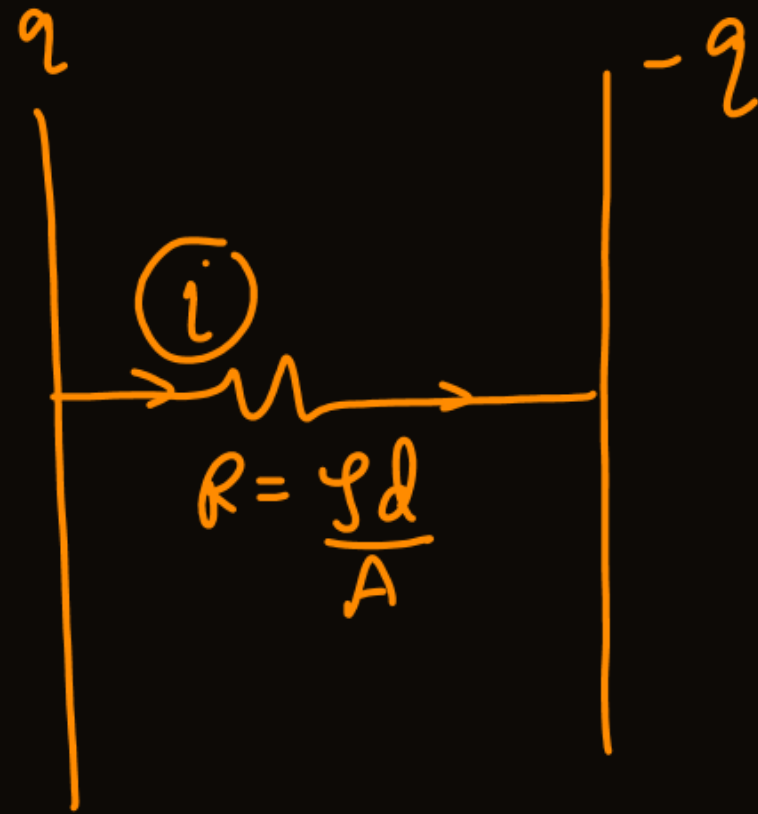

$$i = \frac{2A}{c\gamma d}$$

$$= \frac{qAd}{\kappa A \epsilon \gamma d}$$

$$i = \frac{q}{\kappa \epsilon \gamma} = -\frac{dq}{dt}$$


$$\int_0^t \frac{dt}{\kappa \epsilon \gamma} = \int_q^0 \frac{dq}{q}$$

$$q = Q e^{-\frac{t}{\kappa \epsilon \gamma}}$$

$$= \frac{\kappa A \epsilon V}{d} e^{-\frac{t}{\kappa \epsilon \gamma}}$$

$$i = \frac{AV}{\gamma d} e^{-\frac{t}{\kappa \epsilon \gamma}} \rightarrow \text{Leakage current}$$


①

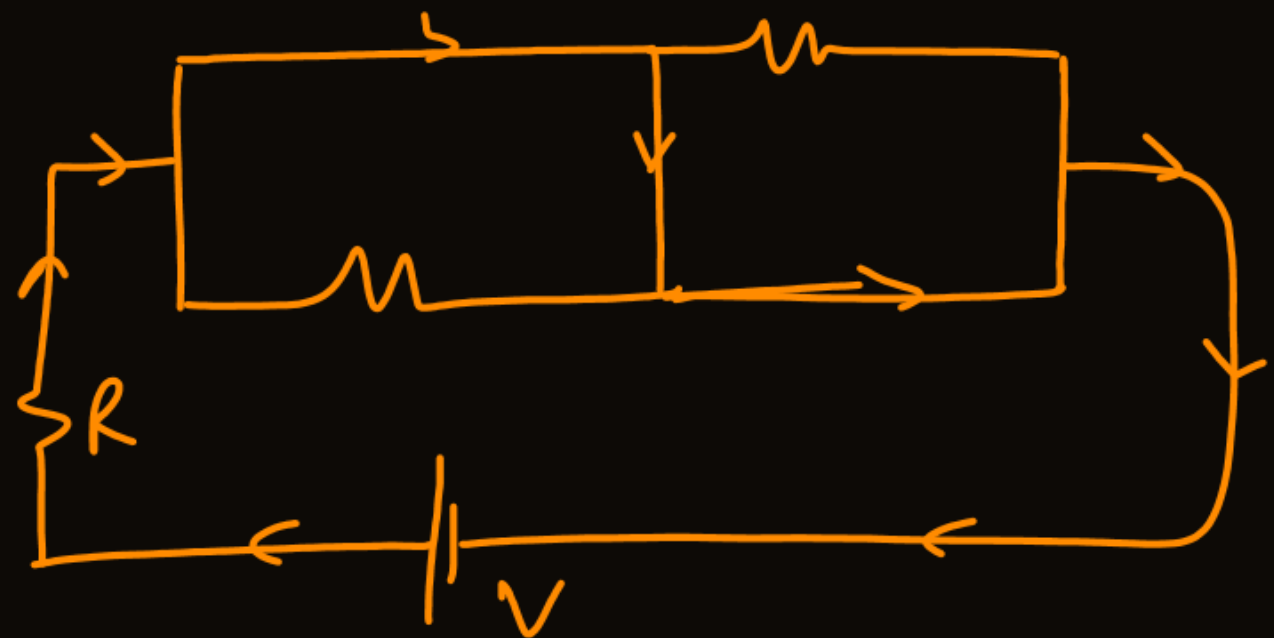

$$R_{eq} = R \Rightarrow i = \frac{V}{R}$$

$$z = \frac{V}{R}$$

②

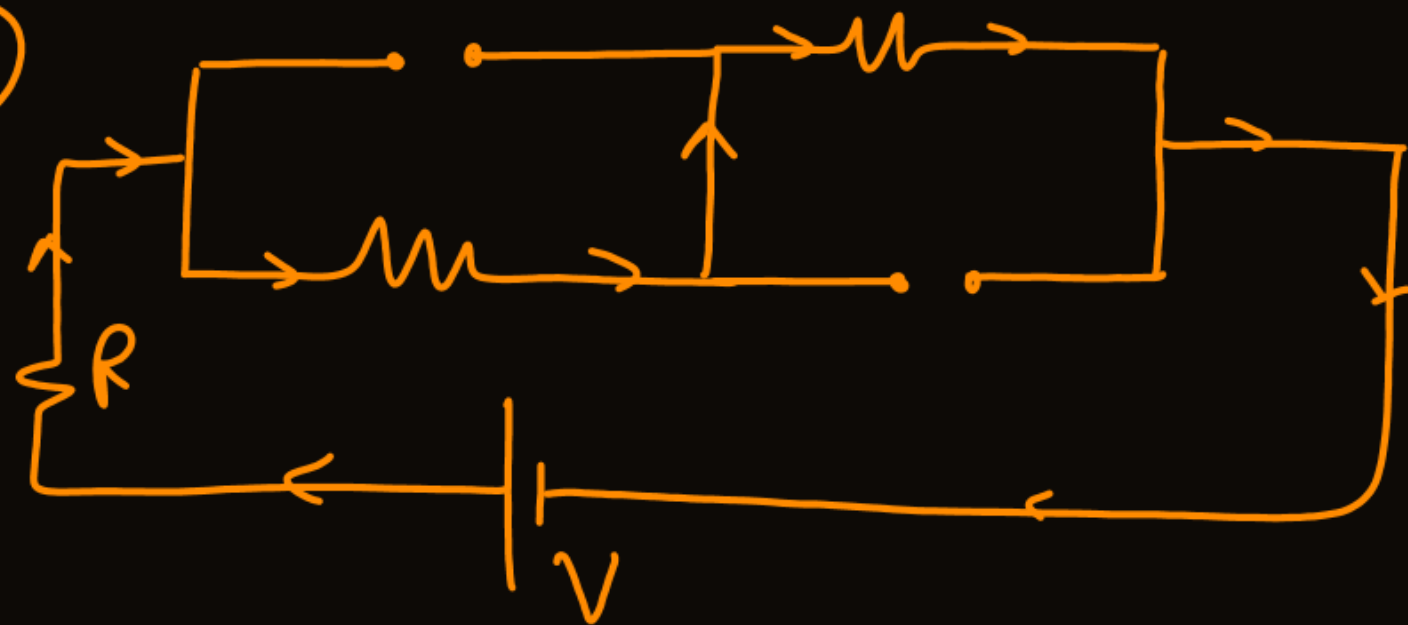


$$R_{eq} = 3R$$

$$i = \frac{V}{3R}$$

$$z = -V/3R$$

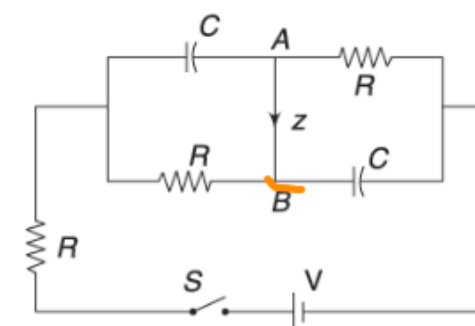Q. 104: In the circuit shown in the fig, the switch 'S' is closed at time $t = 0$. The current in branch AB is represented by z and is taken to be positive when it is from A to B.

- Write the value of z immediately after the switch is closed.
- Write the value of z infinite time after the switch is closed.
- Write z as a function of time (t) and plot the variation of z with time.
- At what time t_0 the current z becomes zero?





$$V = iR + (i-z)R$$

$$V = 2iR - zR \quad \text{--- (1)}$$

$$\frac{z}{C} \frac{dq}{dt} = -\frac{R}{2} \frac{dz}{dt}$$

$$\frac{z}{C} \cdot \frac{i+z}{2} = -\frac{R}{2} \frac{dz}{dt}$$

$$\frac{dq}{dt} = \frac{i+z}{2} \quad \text{--- (2)}$$

$$V - iR - \frac{q^2}{C} \quad \text{--- (3)}$$

$$V - \left\{ \frac{V}{2} + \frac{zR}{2} \right\} = \frac{2q}{C} = \frac{V - zR}{2} \quad \frac{V}{2R} + \frac{z}{2} + z = -\frac{RC}{2} \frac{dz}{dt}$$

$$\frac{V}{2R} + \frac{3z}{2} = -\frac{RC}{2} \frac{dz}{dt}$$

$$-\int_0^t \frac{dt}{RC} = \int_{\frac{V}{R}}^z \frac{dz}{\frac{V}{R} + 3z}$$

$$-\frac{t}{RC} = \frac{1}{3} \ln \left(\frac{V}{R} + 3Z \right)^{\frac{Z}{\frac{V}{R}}}$$

$$t=0 \Rightarrow Z = \frac{V}{R}$$


$$t \rightarrow \infty \quad Z = -\frac{V}{3R}$$

$$-\frac{3t}{RC} = \ln \frac{\frac{V}{R} + 3Z}{\frac{V}{R} + \frac{3V}{R}} = \ln \frac{\frac{V}{R} + 3Z}{4V/R}$$

$$e^{-\frac{3t}{RC}} = \frac{1}{4} + \frac{3Z}{(4V/R)}$$

$$\frac{3Z}{4V/R} = \left(e^{-\frac{3t}{RC}} - \frac{1}{4} \right)$$
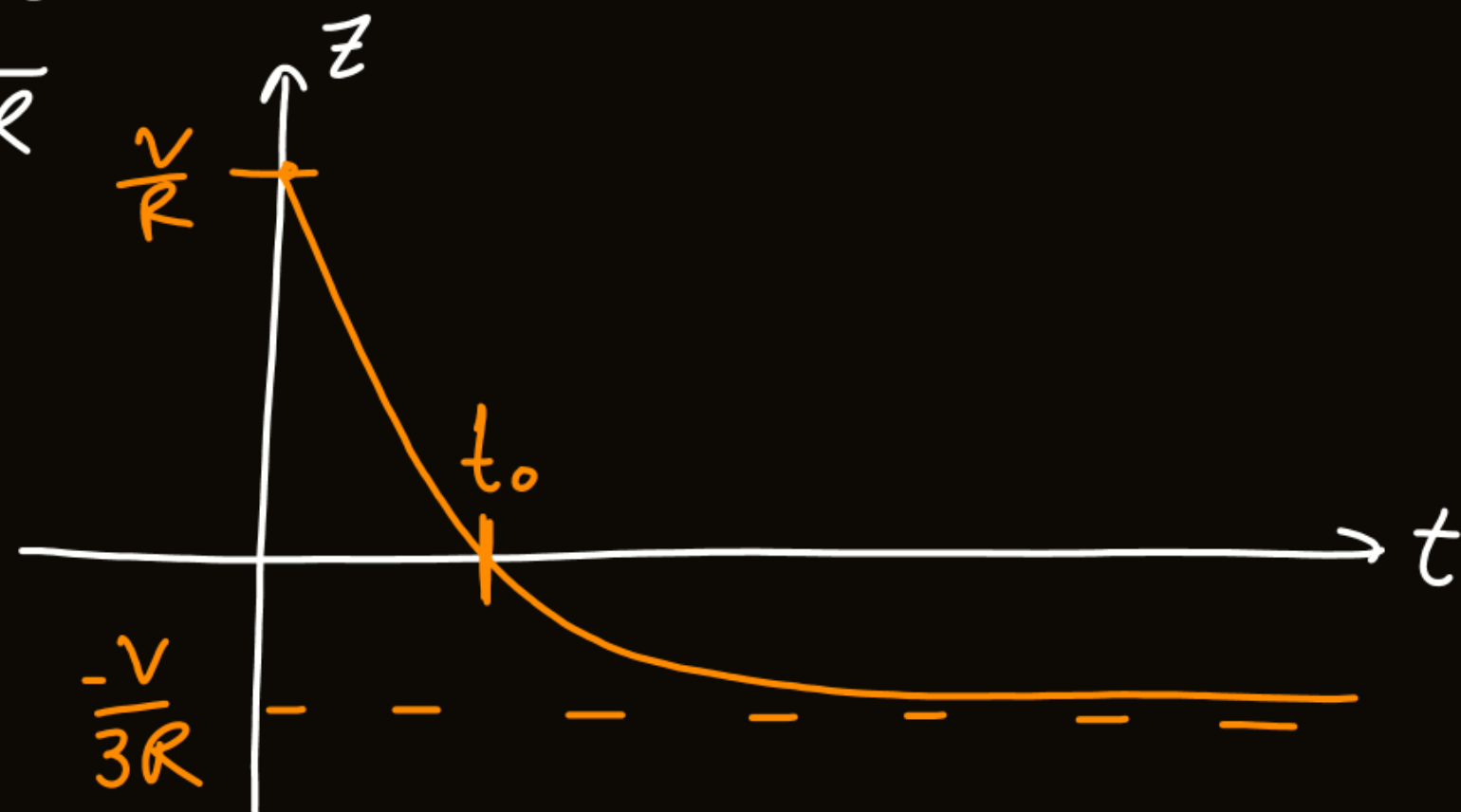
$$Z = \frac{4V}{3R} \left\{ e^{-\frac{3t}{RC}} - \frac{1}{4} \right\}$$



$$e^{-\frac{3t}{RC}} = \ln \frac{1}{4}$$

$$\frac{3t}{RC} = \ln 4 = 2 \ln 2 \Rightarrow$$

$$t_0 = \frac{2RC}{3} \ln 2$$